



17302

21314

3 Hours/100 Marks

Seat No.

--	--	--	--	--	--	--	--	--	--

- Instructions:** (1) **All questions are compulsory.**  
(2) **Illustrate your answers with neat sketches wherever necessary.**  
(3) **Figures to the right indicate full marks.**  
(4) **Assume suitable data, if necessary.**  
(5) **Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.**

MARKS

1. Attempt **any five** : **20**
- a) Draw the energy band diagram for various type of material and compare them (two points).
  - b) Draw the circuit diagram and explain the working of half wave rectifier.
  - c) Draw the symbol of PNP transistor and explain its working.
  - d) Compare RC and LC oscillator.
  - e) Develop the truth table for XOR and XNOR gate. Also draw their symbols.
  - f) With a suitable example explain the concept of primary and secondary transducer.
  - g) List the advantages and disadvantages of mechatronic system.
2. Attempt **any four** : **16**
- a) What is semiconductor ? Explain intrinsic and extrinsic type of semiconductors.
  - b) Develop a circuit for Op-Amp as
    - a) Adder
    - b) Subtractor.
  - c) What is multiplexer ? Draw logical symbol of 4 : 1 multiplexer.
  - d) Explain the selection criteria for the transducer for any application.
  - e) What is PLC ? Draw the block diagram and state the applications of PLC.
  - f) Draw the block diagram of CNC machine and explain its operation.
3. Attempt **any four** : **16**
- a) Explain the following terms :
    - a) Load regulation
    - b) Line regulation.
  - b) Explain RC coupled amplifier with the help of neat diagram.

P.T.O.



- c) What is instrumentation amplifier ? What are its advantages ?
- d) Explain the operation of astable multivibrator using IC 555.
- e) Compare microprocessor and microcontroller (4 points).
- f) Develop a ladder diagram to verify following Bollean equation.
  - i)  $A + B + C = Y$
  - ii)  $A.B.C = X$
  - iii)  $A.B + C = Z$ .

4. Attempt **any four** : 16

- a) Draw the symbol of LDR. Write its working principle and state any two applications.
- b) Explain the need of biasing circuit. List the types of biasing circuits for BJT.
- c) List and explain any four specification of IC 741.
- d) What is flip-flop ? List the types of flip-flop and state its applications (two).
- e) Explain the operation of analog to digital convertor.
- f) State the features of real time mechatronics.

5. Attempt **any four** : 16

- a) List any four criteria for the selection of PLC for an application.
- b) Draw and explain single channel data acquisition system.
- c) What is Half adder ? Draw the logical circuit of half adder along with its truth table.
- d) Draw the circuit diagram of inverting amplifier. Calculate the gain if  $R_f = 12k\Omega$  and  $R_i = 1k\Omega$
- e) Calculate the gain of multistage amplifier if the gain of first stage is 12 dB and gain of second stage is 4 dB.
- f) Compare full wave and half wave rectifier (for any four points).

6. Attempt **any four** : 16

- a) Draw the symbol and list four applications of
    - a) FET
    - b) UJT
  - b) Compare CB and CE configuration for BJT (4 points).
  - c) Draw a labelled pin diagram of IC 555. List its two specifications.
  - d) Sketch 4-bit asynchronous counter.
  - e) Identify active and passive transducers from the list below.
    - a) Thermocouple
    - b) RTD
    - c) Strain gauge
    - d) Piezoelectric crystal
  - f) With the help of neat labelled diagram explain FMS.
-