

17638

15116

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--	--	--

- Instructions –*
- (1) All Questions are *Compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.
 - (8) Use of Steam tables, logarithmic, Mollier's chart is permitted.

	Marks
1. a) Answer any <u>THREE</u> of the following:	12
(i) Draw the symbols of - 1) SCR 2) GTO 3) IGBT 4) TRIAC (ii) State the necessity of converters and give the classification of controlled converters.	

- (iii) Draw and explain the working of single phase half bridge inverter.
- (iv) Draw and explain the working of DC static circuit breaker.

b) Answer any ONE of the following:

06

- (i) Draw a neat circuit diagram of parallel inverter. Explain its working with necessary waveforms.
- (ii) Draw a neat circuit diagram 1ϕ fully controlled bridge rectifier with RL load. Explain the working with waveforms.

2. Answer any FOUR of the following:

16

- a) Draw the V-I characteristics of SCR. Define:
- (i) latching current
 - (ii) holding current
- b) Compare single phase and three phase converter on the basis of
- (i) RMS voltage
 - (ii) average voltage
 - (iii) ripple factor
 - (iv) efficiency
- c) Draw and explain the working of 1ϕ half wave controlled rectifier with RL load. Explain the effect of four wheeling diode.
- d) State the classification of choppers.
- e) Describe the speed control by dc series motor using single phase half controlled bridge converter.
- f) With a neat circuit explain the operation of step up chopper.

3. Answer any FOUR of the following: **16**

- a) Describe $\frac{dv}{dt}$ triggering of SCR.
- b) Define firing angle and conduction angle. Find the value of firing angle so as to get a conduction angle of 135° .
- c) Describe the four specifications of SCR.
- d) Draw and explain a Jones chopper.
- e) Describe automatic street lighting circuit using SCR.

4. a) Answer any THREE of the following: **12**

- (i) Draw and explain the operations of class C chopper.
- (ii) Explain pulse gate triggering of SCR.
- (iii) Draw and explain the working of a chopper controlled dc drive (step down)
- (iv) Define duty cycle of a chopper. Explain various control techniques used in chopper.

b) Answer any ONE of the following: **06**

- (i) Describe the operation of 3ϕ series inverter with c/p-o/p waveforms and circuit diagram.
- (ii) Draw and explain a 3ϕ fully controlled bridge converter with R load. Explain the working with waveforms.

5. Answer any FOUR of the following: **16**

- a) Describe the principle of dielectric heating. State two applications of it.
- b) With necessary circuit explain auxiliary commutation in chopper.
- c) Describe harmonic reduction by single pulse width modulation.
- d) Draw and explain electric welding control circuit using SCR.
- e) State the methods of o/p voltage control of inverters. Explain PWM control in detail.
- f) Draw and explain modified series inverter.

6. Answer any FOUR of the following: **16**

- a) Draw the circuit diagram of class E-chopper and explain its working.
 - b) Explain the principle of static VAR compensation.
 - c) Compare induction heating and dielectric heating on the basis of
 - (i) material
 - (ii) rate of heating
 - (iii) frequency
 - (iv) applications
 - d) Explain the two transistor model of SCR.
 - e) State the speed control methods of 3ϕ induction motor. Explain variable frequency control.
-