



17215

21314

3 Hours/100 Marks

Seat No.

--	--	--	--	--	--	--	--	--	--

-
- Instructions:** (1) **All questions are compulsory.**
(2) **Illustrate your answers with neat sketches wherever necessary.**
(3) **Figures to the right indicate full marks.**
(4) **Assume suitable data, if necessary.**
-

MARKS

1. Attempt **any ten** of the following : **20**
- a) Draw symbols of Schottky diode and Tunnel diode.
 - b) Define permeability and reluctance of magnetic material.
 - c) State different types of filters.
 - d) List two applications of LDR.
 - e) Define Rectifier. List its types.
 - f) List any two applications of photodiode and IRLED.
 - g) State the necessity of waveshaping circuits.
 - h) State Kirchoffs current law along with its formula.
 - i) List any four applications of Laser diode.
 - j) Draw ideal current source and practical current source.
 - k) Define rectification efficiency. Give its formula.
 - l) Draw circuit diagram of RC differentiator. Write expression for output.
 - m) List any four dielectric materials used in manufacturing the capacitor.
 - n) State superposition theorem.
2. Attempt **any four** of the following : **16**
- a) Describe NTC and PTC resistors with temperature resistance characteristics.
 - b) Describe the working of PN junction diode with neat sketch under forward biased condition.
 - c) Draw the constructional diagram of iron core inductor. List applications.
 - d) Describe construction of Aluminium Electrolytic capacitor.
 - e) Draw the circuit diagram for centre tap full wave rectifier with LC filter. Draw its input and output waveforms.
 - f) Describe the working of positive clamper with neat circuit diagram and input/output waveforms.

P.T.O.



3. Attempt **any four** of the following :

16

- a) Write color codes for following resistors.
 - i) $470\text{ k}\Omega \pm 5\%$
 - ii) $1.2\text{ M}\Omega \pm 10\%$.
- b) Define following terms in case of PN junction diode :
 - i) Static resistance
 - ii) Dynamic resistance
 - iii) Cut-in voltage
 - iv) Breakdown voltage.
- c) Draw construction of PVC gang capacitor and describe its working.
- d) Compare HWR and FWR (any four points).
- e) Draw construction of Tunnel diode. Describe its working.
- f) Identify the following circuit. Draw its input/output waveforms. (Refer Figure 1)

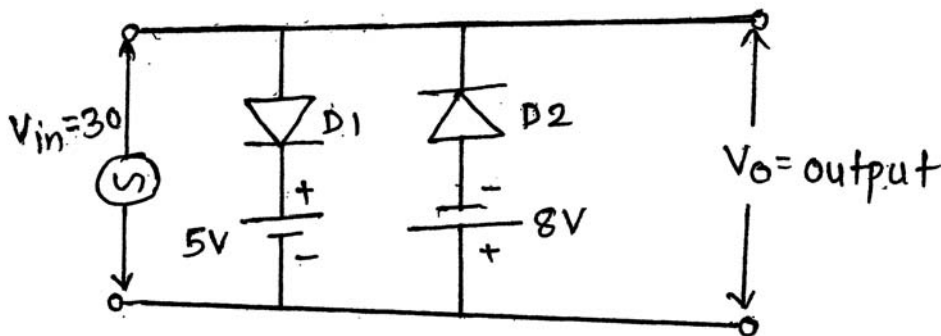


Figure : 1 [Q. 3(f)]

4. Attempt **any four** of the following :

16

- a) Draw VI characteristics of zener diode. List its two specifications.
- b) Draw construction of LED and explain its working.
- c) Draw circuit diagram for RC integrator. Write expression for output voltage. Draw output waveform for square wave as input.
- d) In full wave bridge rectifier load resistance $R_L = 2\text{ k}\Omega$. The diode has forward bias dynamic resistance of 10Ω . If AC voltage across secondary winding of transformer is $V = 100 \sin 314t$. Determine
 - i) Peak value of current (I_m)
 - ii) DC value of voltage (V_{dc})
 - iii) DC value of current (I_{dc})
 - iv) PIV.



MARKS

- e) Compare soft magnetic materials and hard magnetic materials. (For four points.)
- f) Calculate equivalent resistance R_{AB} using delta-star transformation (Refer Figure : 2)

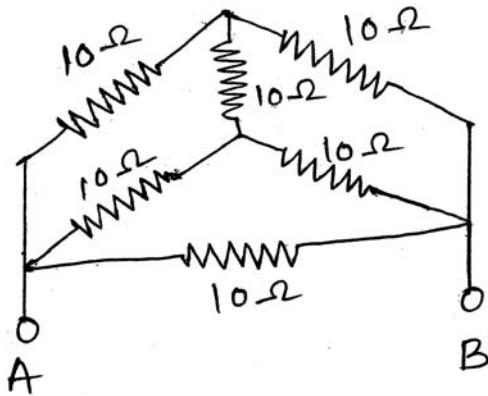


Figure : 2 [Q. 4(f)]

5. Attempt **any four** of the following :

16

- a) Describe the meaning of the term open circuit and short circuit with neat diagram.
- b) Compare LED and PN junction diode (any four points).
- c) Define following terms in case of rectifier
 - i) Ripple factor
 - ii) TUF
 - iii) Ripple frequency
 - iv) PIV.
- d) Compare clipper and clampers by any four points.
- e) State and explain Thevenien's theorem with suitable example.
- f) Calculate the value of current in 5Ω resistor. Using Norton's theorem for a network as shown. (Refer figure : 3)

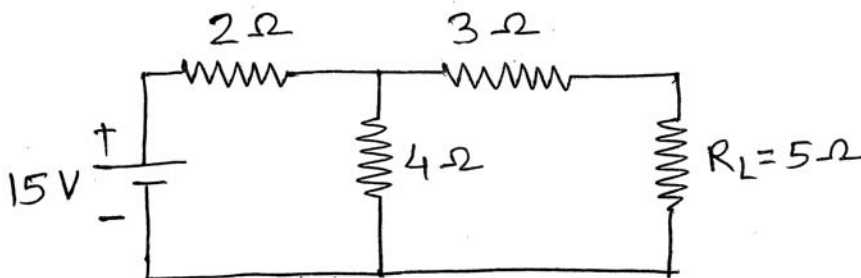


Figure : 3 [Q. 5(f)]



6. Attempt **any four** of the following :

16

a) Define following terms :

- i) Active network ii) Passive network
 iii) Linear network iv) Non-linear network

b) Describe avalanche and zener breakdown of PN junction.

c) Draw the circuit diagram of bridge rectifier with π Filter. Describe its working. Draw input/output waveforms.

d) With the help of circuit diagram, input/output waveforms describe operation of negative shunt clipper.

e) Calculate current flowing through 6Ω resistor using KVL. (Refer Figure : 4)

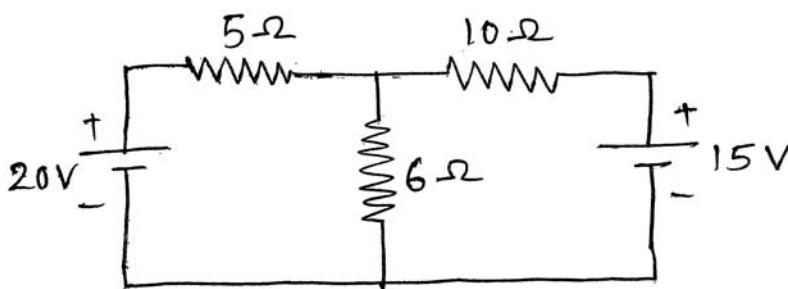


Figure : 4 [Q. 6(e)]

f) Calculate value of R_L , so that power transferred is maximum in the circuit shown in figure. (Refer Figure : 5)

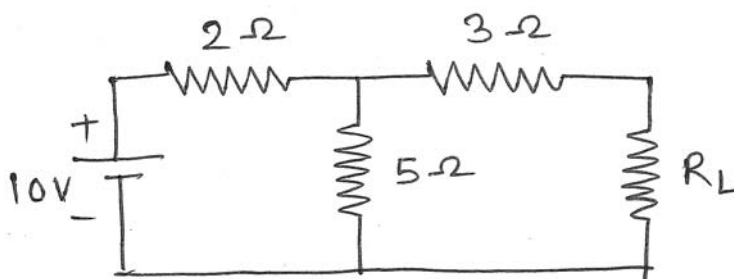


Figure : 5 [Q. 6(f)]