

17445

21314

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* – (1) All Questions are *Compulsory*.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data, if necessary.
- (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
- (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.
- (7) Preferably write the answers in sequential order.

Marks

1. a) Attempt any **SIX** of the following: **12**
- i) Draw ideal and practical transfer characteristics of op-Amp.
- ii) Draw block diagram of op-Amp. State function of each block.
- iii) Draw pin diagram of IC LM324.
- iv) State functions of following pins of IC555
- 1) Control
- 2) Trigger
- v) State the function of filter. Draw response of high pass filter.

P.T.O.

- vi) Draw inverting zero crossing detector and its waveforms with circuit diagram.
- vii) Compare open loop and closed loop configuration on basis of
 - 1) Gain
 - 2) Bandwidth.
- viii) Define sample and hold period with reference to S/H circuit.

b) Attempt any **TWO** of the following:

08

- i) Draw circuit diagram to generate the following output using op-Amp: $V_0 = 3V_1 + 2V_2 - 4V_3$.
 V_1, V_2, V_3 are input voltages.
- ii) Draw single i/p balanced o/p differential amplifier and define the term balanced o/p and unbalanced o/p.
- iii) Draw block diagram of frequency multiplier and describe its working using PLL.

2. Attempt any **FOUR** of the following:

16

- a) Draw instrumentation amplifier using 3 op-Amps. State its voltage gain equation.
- b) Draw closed loop Inverting amplifier and derive expression for voltage gain.
- c) State ideal and typical value of the following parameters of IC741.
 - i) Supply voltage rejection ratio SURR
 - ii) Common mode rejection ratio (CMRR)
 - iii) Slew rate
 - iv) Unity gain bandwidth.

- d) Draw basic integrator and derive the expression for its output voltage.
- e) Draw circuit diagram of V-I converter of floating load. Derive expression for its output.
- f) Draw circuit diagram of astable M/V using IC555. State its frequency equation, duty cycle, time period.

3. Answer any FOUR of the following:

16

- a) Draw phase shift oscillator using IC741. Explain the function of each component in it. State the equation for o/p frequency.
- b) Describe the concept of virtual ground with reference to op-Amp.
- c) Draw window detector using op-Amp and give transfer characteristics.
- d) Compare comparator and schmitt trigger on basis of
 - i) Definition
 - ii) Feedback
 - iii) Hysteresis
 - iv) External reference voltage.
- e) What do you mean by active filter. State its advantages over passive filters (any two). Define passband and stop band w. r. to filters.
- f) Draw and explain operation of phase detector.

4. Attempt any **FOUR** of the following:


16

- Design second order butterworth high pass filter of cut off frequency 10KHz.
- Draw block diagram of PLL as a FM demodulator. Explain function of each block.
- Draw circuit diagram of a logarithmic amplifier. State its equation for output voltage.
- Compare active integrator and active differentiator on basis of
 - Output voltage
 - Feedback element
 - Application in filter.
 - Gain
- Draw and explain touch plate switch using IC555.
- Draw I-V converter using op-Amp. Derive expression for its output voltage.

5. Attempt any **FOUR** of the following:

16

- Draw circuit diagram of op-Amp based filter circuit which provides the following response. Describe its operation. (Refer Figure No. 1)

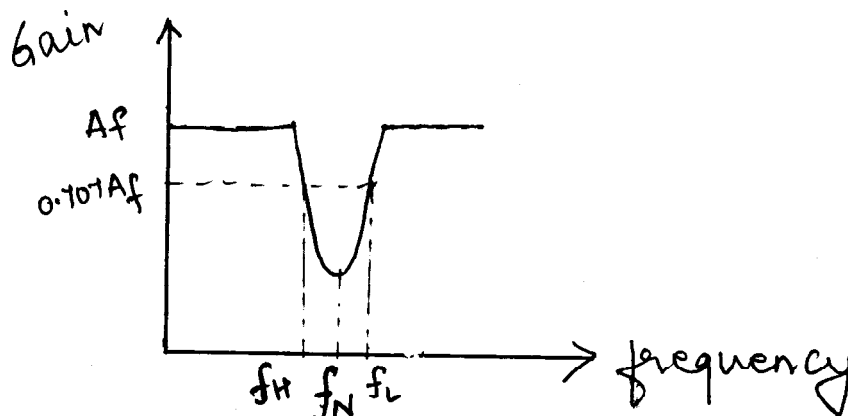Fig. No. 1

- b) Determine pulse width of monostable M/V using IC555 timer for $c = 0.047\mu\text{F}$ and $R = 56\text{K}$.
- c) For the given circuit, obtain the output voltage.
(Refer Figure No. 2)

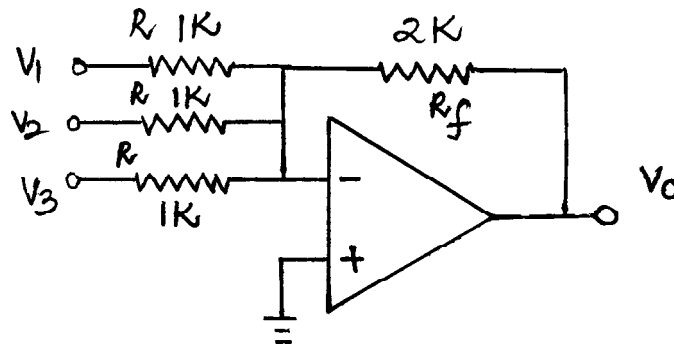


Fig. No. 2

- d) Draw and explain operation of wide band filter with help of circuit diagram.
- e) Identify the circuit, redraw it. Draw the o/p of the circuit.
State how will you obtain it. (Refer Figure No. 3)

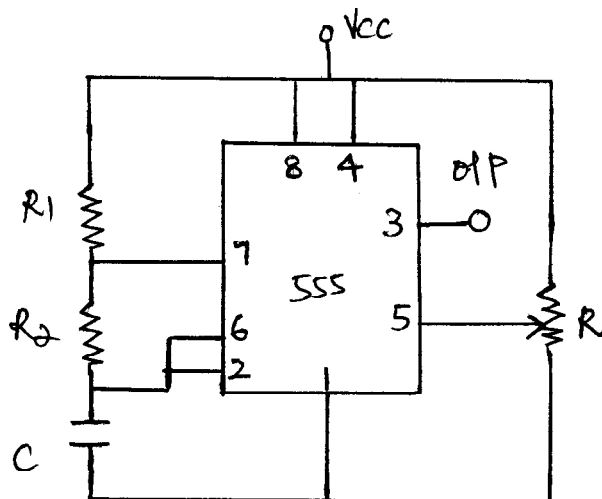


Fig. No. 3

- f) State the need of peak to peak detector. Draw circuit diagram.

6. Attempt any FOUR of the following:**16**

- a) Design a circuit to obtain the output voltage $V_0 = 10(V_1 - V_2)$.
 - b) What is PLL. Explain its operation with a block diagram.
 - c) Define Multivibrator. State the types of multivibrator. Which M/V can be used as a flipflop. Draw the circuit diagram.
 - d) Draw circuit diagram of first order low pass filter. Give expression of cut off frequency and gain.
 - e) For a schmitt trigger with op-Amp find Threshold Voltage V_{UTP} and V_{LTP} when $R_2 = 150K\Omega$, $R_1 = 100K\Omega$, $V_{in} = 500mV$, Sine wave saturation voltage = $\pm 15V$. Also find hysteresis voltage.
 - f) Define:
 - i) Input offset voltage.
 - ii) Input offset current.
 - iii) Input bias current.
 - iv) Output offset voltage.
-