

22213

12526

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* – (1) All Questions are *Compulsory*.
- (2) Answer each next main Question on a new page.
- (3) Illustrate your answer with neat sketches wherever necessary.
- (4) Figures to the right indicate full marks.
- (5) Assume suitable data, if necessary.
- (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
- (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

- 1. Attempt any FIVE of the following: **10****
- a) Draw the symbol of :–
- i) Zener diode
- ii) Photo diode.
- b) List any two applications of P-N junction diode.
- c) State different types of rectifiers.
- d) Draw common base configuration of transistor.
- e) Define :–
- i) Line regulation
- ii) Load regulation.
- f) State the IC number to provide fixed output voltage of +5V and –12V.
- g) Draw the logic symbol and truth table of Ex-NOR gate. P.T.O.

- 2. Attempt any THREE of the following:** **12**
- a) With neat diagram describe the working principle of LASER diode.
 - b) Sketch Input and Output waveforms of centre tapped fullwave rectifier.
 - c) Draw and explain output characteristics of CE configuration of transistor.
 - d) Draw block diagram of DC regulated power supply. State the function of each block.
- 3. Attempt any THREE of the following:** **12**
- a) Compare Half wave and Full wave rectifier on the following basis :-
 - i) PIV
 - ii) Ripple factor
 - iii) Efficiency
 - iv) TUF.
 - b) Describe the working of NPN transistor.
 - c) List the features of IC 723 voltage regulator. (Any eight)
 - d) Compare LC and RC oscillators. (Any four points)
- 4. Attempt any THREE of the following:** **12**
- a) Differentiate between LED and Photo diode. (Any four points)
 - b) Describe with neat circuit diagram working of LC filter with bridge rectifier.
 - c) Define filter list the types of filter.
 - d) Explain how transistor works as a switch?
 - e) Draw a neat circuit diagram of crystal oscillator. For a crystal oscillator circuit $L = 0.01 \text{ H}$ and $C = 10 \text{ PF}$. Find the frequency of oscillation.

5. Attempt any TWO of the following:**12**

- a) Compare CB, CE and CC configurations of transistor on the following basis :-
- i) Input resistance
 - ii) Output resistance
 - iii) Voltage gain
 - iv) Current gain
 - v) Phase shift
 - vi) Application.
- b) Sketch functional block diagram of IC 723 and explain each block.
- c) Implement all basic gates using NAND gate.

6. Attempt any TWO of the following:**12**

- a) Define α and β of transistor. Derive relation between α and β .
- b) Sketch and describe working of colpitt's oscillator. List any two applications of colpitt's oscillator.
- c) State and prove De-Morgan's first and second theorem.
-