



22216

12223

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.

Marks

1. Attempt any FIVE of the following :

10

- (a) Draw the constructional diagram of LED and label it.
- (b) State the working principle of photodiode.
- (c) Define Operating point and give its significance.
- (d) List two applications of FET.
- (e) Name two types of JFET & draw their symbols.
- (f) Draw the circuit of Zener diode as voltage regulator.
- (g) State the advantages of transistorized regulator.



2. Attempt any THREE of the following :**12**

- (a) Define Energy band and state the effect of temperature on it for a semiconductor with an example.
- (b) Draw the circuit diagram of transistor in CE configuration and explain its output characteristics.
- (c) Draw the circuit of base bias with emitter feedback and describe its operation.
- (d) Draw the block diagram of DC regulated power supply and describe the working of each block.

3. Attempt any THREE of the following :**12**

- (a) A full wave rectifier uses two diodes, the internal resistance of each diode may be assumed constant at 20Ω . The transformer r.m.s. secondary voltage from centre tap to each end of secondary is 50 V and load resistance is 980Ω .

Find :

- (i) D.C. load current
 - (ii) r.m.s. value of load current.
- (b) Define the following terms :
 - (i) PIV
 - (ii) Efficiency
 - (iii) Ripple factor
 - (iv) TUF
 - (c) Draw the output characteristics of JFET and describe the salient points related to it.
 - (d) Draw the circuit of transistorized series voltage regulator and explain its operation.

4. Attempt any THREE of the following :

12

- (a) Compare between LC filter and π filter on the basis of :
- Load regulation
 - Ripple factor
 - Suitable for type of load
 - Components used
- (b) Explain the terms w.r.t. BJT biasing :
- Stabilization
 - Thermal runaway
- (c) Calculate the emitter current in the voltage divider circuit shown in Fig. 4(c). Also find the value of V_{CE} and collector potential V_C .

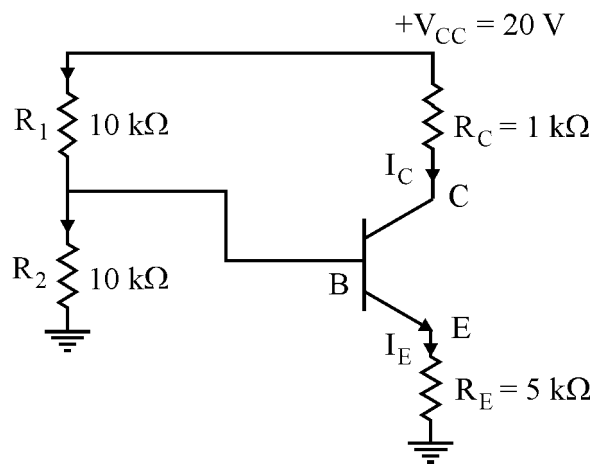


Fig. 4 (c)


- (d) Compare between source self bias and drain to source bias. (any 4 points).
- (e) Describe the terms :
- Load regulation
 - Line regulation

5. Attempt any TWO of the following :


12

- (a) State the working principle of E-MOSFET and draw and explain its constructional sketch.

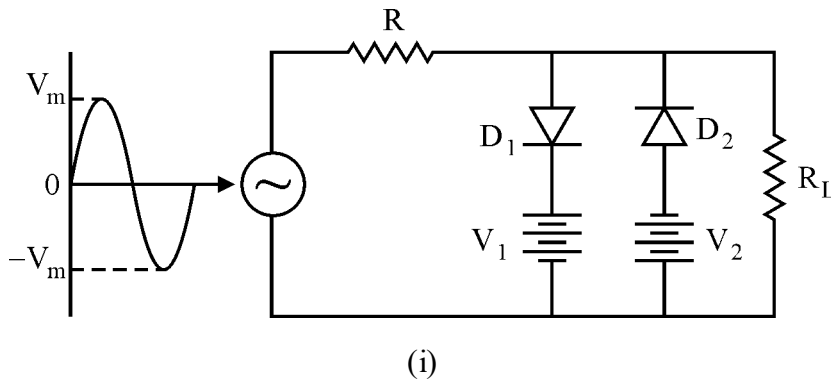- (b) Identify the circuit in Fig. 5(b) (i) & (ii) and draw the input and output waveforms.



(i)
Fig. 5 (b)

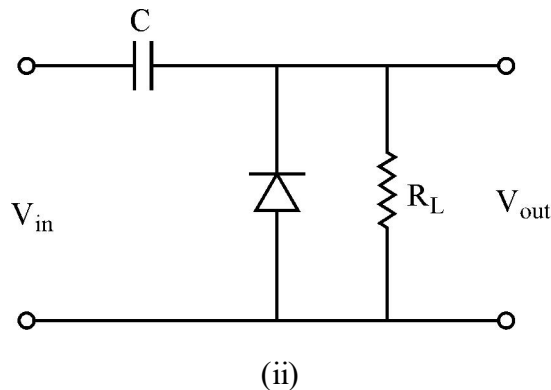

(ii)
Fig. 5 (b)

- (c) Draw the V-I characteristics of Zener diode in reverse bias and explain it.

6. Attempt any TWO of the following :

12

- Draw and explain forward and reverse V-I characteristics of PN junction diode and justify their use as rectifier.
- Draw the bridge rectifier circuit. Describe its working with the input and output waveforms.
- Justify the use of CE configuration in transistor amplifiers with respect to their DC load line & operating point.

