

22225

12223

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.

Marks**1. Attempt any FIVE of the following :****10**

- (a) Define Active and Passive Components.
- (b) Draw V-I characteristics of an ideal P-N junction diode.
- (c) Define Rectifier. List the types of Rectifiers.
- (d) Define α and β of Transistor.
- (e) Define transducers and name any two active transducers.
- (f) Draw constructional diagram of a photodiode.
- (g) State two advantages of Integrated circuits.



- 2. Attempt any THREE of the following : 12**
- (a) List the types of signals. State the expression for frequency f and wavelength λ , of an A.C. signal.
 - (b) Derive the relationship between α and β of transistor.
 - (c) State and explain the operating principle of P-N junction diode under forward bias condition.
 - (d) Draw the construction of Cup Type LED. List any two applications of it.
- 3. Attempt any THREE of the following : 12**
- (a) Compare FET and BJT (Any Four points).
 - (b) Explain the working principle of phototransistor. State any two advantages of phototransistor.
 - (c) Determine the value of resistance with following colour code :
 - (i) Brown Black Black Silver
 - (ii) Red Red Orange Gold
 - (d) Describe the working principle of n-p-n transistor with the help of neat diagram.
- 4. Attempt any THREE of the following : 12**
- (a) State any four selection criteria for transducers.
 - (b) Define the following terms with respect to Rectifier :
 - (i) Ripple Factor
 - (ii) Rectification Efficiency (h)
 - (iii) Transformer Utilization Factor (TUF)
 - (iv) Peak Inverse Voltage (PIV)

- (c) Draw the circuit diagram of single stage RC coupled CE amplifier. State any two advantages of it.
- (d) Draw and explain Drain characteristics of n-channel JFET.
- (e) Draw and explain the working of CLC filter.

5. Attempt any TWO of the following :

12

- (a) Calculate peak to peak amplitude, Frequency and wavelength of waveforms shown in Figure-1.

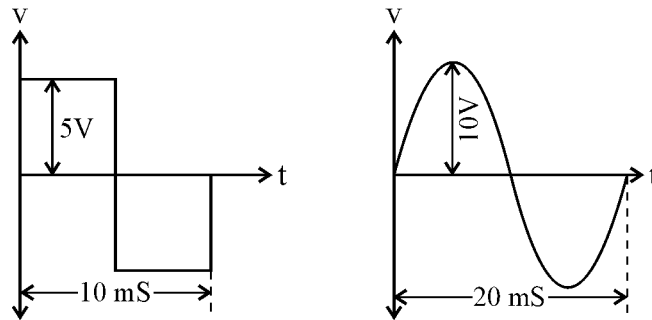


Figure – 1

- (b) In CE configuration of transistor, if $\beta = 50$, leakage current $I_{CEO} = 100 \mu\text{A}$. If the Base current is 0.2 mA. Calculate the value of I_C , I_E and α .
- (c) (i) Sketch the Full Wave Bridge Rectifier and draw the waveforms of Load Voltage and Load Current.
- (ii) State any two advantages of FWR over HWR.

6. Attempt any TWO of the following :

12

- (a) (i) A JFET has a drain current of 10 mA. If $I_{DSS} = 20 \text{ mA}$ and $V_{GS}(\text{off}) = -8\text{V}$. Find the value of: (i) V_{GS} (ii) V_P
- (ii) Draw the symbol of N-channel and P-channel MOSFET.

(b) Observe the given frequency response of RC coupled amplifier, shown in Figure-2. Calculate :

- (i) Lower cutoff frequency (f_L)
- (ii) Higher cutoff frequency (f_H) and
- (iii) Bandwidth (BW)

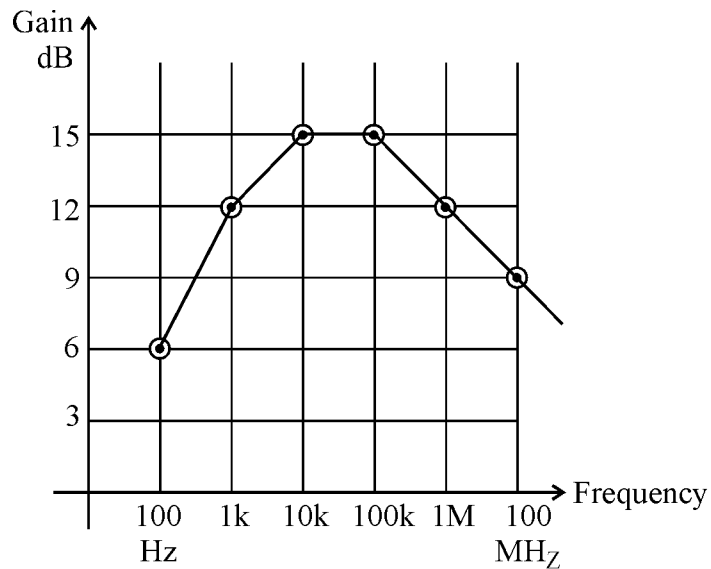


Figure – 2

(c) List four types of electrical pressure transducers and state one application of each type.

