

22225

12526

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

-
- Instructions* – (1) All Questions are *Compulsory*.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data, if necessary.
- (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
- (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

- 1. Attempt any FIVE of the following :** **10**
- a) Define the terms –
- i) Amplitude
- ii) Frequency
- b) State the need of filters and list any two types of filter.
- c) Draw labelled symbol for N-Channel and P-Channel FET.
- d) Draw neat sketch for input characteristics of CE configuration.
- e) State any two selection criteria for transducer.
- f) Give any two points of comparison between Active and Passive transducer.
- g) List any two advantages of Integrated circuits.

P.T.O.

2. Attempt any THREE of the following : 12
- State different types of resistor.
 - Compare BJT and FET.
 - Sketch the labelled forward and reverse characteristic of P-N junction diode.
 - Explain working principle of Half wave rectifier.
3. Attempt any THREE of the following : 12
- Determine the value of resistance with the following colour code –
 - Brown Black Black Silver
 - Red Red Orange Gold
 - Draw a neat sketch of piezoelectric transducer and describe the working of the same.
 - Draw and explain construction of N-Channel JFET with diagram.
 - Draw the circuit of single stage R-C amplifier and state the function of coupling capacitor and Emitter bypass capacitor used in circuit.
4. Attempt any THREE of the following : 12
- In CE configuration if $\beta = 100$, leakage current $I_{CEO} = 150 \mu\text{A}$ and if the base current is 0.2 mA. Calculate value of I_C , I_E .
 - Explain –
 - Seebeck and
 - Peltier effect
 - Draw the block diagram of regulated power supply and explain working of each block.
 - Draw and explain with diagram L-C filter in detail.
 - A JFET has a drain current of 10 mA. If $I_{DSS} = 20 \text{ mA}$ and $V_{GS(\text{off})} = -8\text{V}$. Find the value of–
 - V_{GS} and
 - V_p

5. Attempt any TWO of the following :

12

- Define terms α and β of transistor and derive the relation between α and β .
- Calculate peak to peak amplitude, frequency and wavelength of waveforms shown in Fig. No. 1(a) (b).

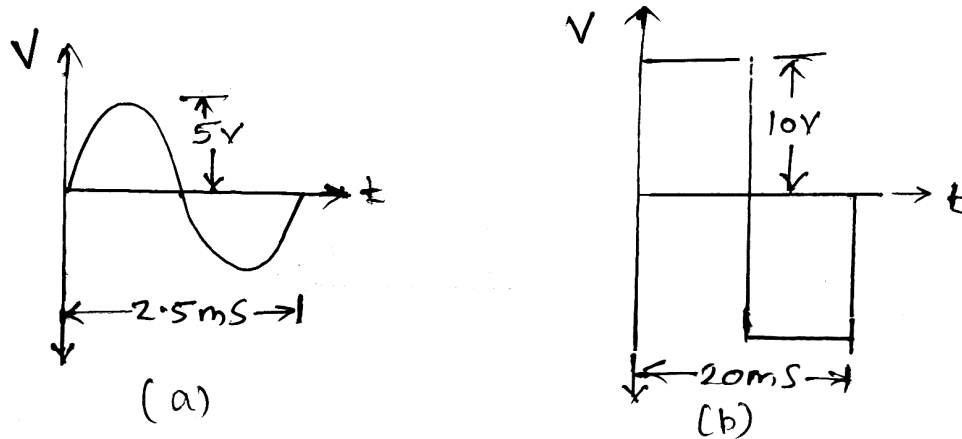


Fig. No. 1(a) (b)

- Identify the given circuit shown in the Fig. No. 2 and explain working with input - output waveforms for a sinusoidal input.

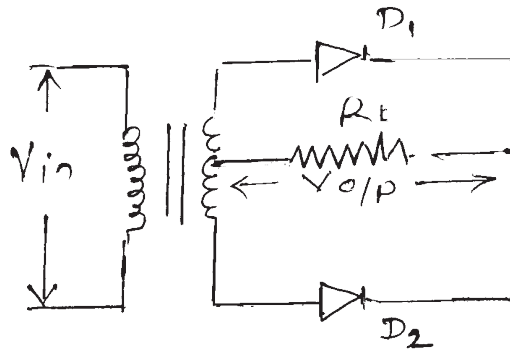


Fig. No. 2

6. Attempt any TWO of the following :**12**

- a) State the terms related to field effect transistor –
 - i) Drain resistance
 - ii) Transconductance
 - iii) Amplification factor
 - b) Differentiate CB, CE and CC w.r.t. points –
 - i) Input resistance
 - ii) Output resistance
 - iii) Current gain
 - iv) Phase shift between input and output.
 - c) Identify the active and passive transducer from the following :
 - i) Capacitive transducer
 - ii) Thermistor
 - iii) Photovoltaic cell
 - iv) Thermocouple
 - v) Strain guage
 - vi) Piezoelectric transducer
-