

22232

11920

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Illustrate your answers with neat sketches wherever necessary.
  - (3) Figures to the right indicate full marks.
  - (4) Assume suitable data, if necessary.

**Marks**

**SECTION – I**

**1. Attempt any SIX of the following :**

**12**

- (a) Define the terms :
  - (i) EMF
  - (ii) Potential difference
- (b) State the Faraday's law of electromagnetic induction.
- (c) Define :
  - (i) Angular velocity
  - (ii) Power factor
- (d) Define transformation ratio of transformer & efficiency of transformer.
- (e) Define RMS value & Average value with respect to sinusoidal AC waveform.
- (f) Draw RL series circuit.
- (g) State the types of FHP motor.

**2. Attempt any THREE of the following :**

**12**

- (a) Draw & explain B-H curve.
- (b) Explain the working of single phase AC motor.
- (c) Draw & explain RLC series circuit.
- (d) Explain the working principle of Auto-transformer.


[1 of 4]

P.T.O.

3. Attempt any TWO of the following :

12

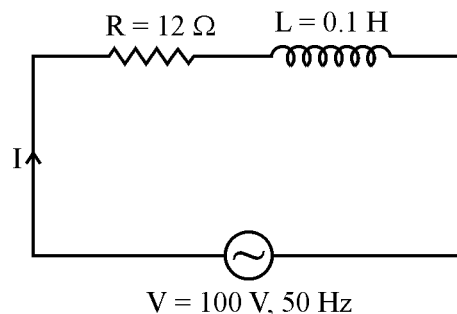- (a) Derive the EMF equation of single phase transformer. State the losses in transformer.
- (b) Define self-induced emf & mutually induced emf. Derive the equation of self inductance & mutual inductance.
- (c) A coil having resistance of  $12 \Omega$  & an inductance of  $0.1\text{H}$  is connected across a  $100 \text{ V}$ ,  $50 \text{ Hz}$  supply; calculate :
  - (i) the reactance & impedance of coil
  - (ii) the current



#### SECTION – II

4. Attempt any FIVE of the following :

10

- (a) Give examples of active component & passive component.
- (b) State the configurations of BJT.
- (c) Define efficiency & ripple factor of rectifier.
- (d) Define  $\alpha$  (alpha) and  $\beta$  (beta) of a transistor.
- (e) Draw V-I characteristics of p-n junction diode & give rated value of cut-in-voltage for Si & Ge.
- (f) State the need of filter in DC regulated power supply.

**5. Attempt any THREE of the following : 12**

- (a) Explain the construction & working of LED.
- (b) Compare Common Base (CB), Common Emitter (CE) & Common Collector (CC) configuration of BJT.
- (c) Explain voltage source & current source with diagram.
- (d) Draw the following signals & explain the parameters of each signal :
  - (i) Sinusoidal
  - (ii) Square

**6. Attempt any TWO of the following : 12**

- (a) Calculate value of resistor from the given colour codes :
    - (i) Brown Black Red Gold
    - (ii) Yellow Violet Orange Gold
    - (iii) Red Red Orange Silver
  - (b) Draw a circuit diagram of full wave centre tap rectifier with capacitor filter & explain the operation with waveforms.
  - (c) Draw & explain transistor as an amplifier. State the effect of cascading on voltage gain & bandwidth.
-

