

22320

21222

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

15 minutes extra for each hour

- Instructions* – (1) All Questions are *Compulsory*.
- (2) Answer each next main Question on a new page.
- (3) Illustrate your answers with neat sketches wherever necessary.
- (4) Figures to the right indicate full marks.
- (5) Assume suitable data, if necessary.
- (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

- 1. Attempt any FIVE of the following: **10****
- a) Convert $(1101011)_2 = (\quad)_{16}$ and
 $(1111011)_2 = (\quad)_8$
- b) List triggering methods used for triggering flip flops.
- c) Define Minterm and Maxterm w.r.t. K-map.
- d) Define shift register and list its types.
- e) List any two specifications of IC-DAC 0808.
- f) Draw logical circuit diagram of half adder circuit.
- g) Write truth table of D type flip-flop.

P.T.O.

- 2. Attempt any THREE of the following:** **12**
- a) Convert $(43)_{10} = (\text{BCD})$
 $(34)_{10} = (\text{Excess-3})$
 $(110111)_2 = (\text{Gray})$
 $(11101)_2 = (2\text{'s complement})$
 - b) Draw logical diagram of full adder using K-map simplification and write truth table.
 - c) Draw the block diagram of programmable logic Array with proper labels.
 - d) Draw the circuit diagram of BCD to 7 - segment decoder and write truth table.
- 3. Attempt any THREE of the following:** **12**
- a) State and prove two De-Morgan's Theorems.
 - b) Draw basic gates AND, OR and NOT using NAND gate only.
 - c) Draw 4 bit ring counter with truth table and its waveform.
 - d) Compare the following: (Any two points each)
 - (i) Volatile - Non volatile memory
 - (ii) SRAM - DRAM memory
- 4. Attempt any THREE of the following:** **12**
- a) Realize given boolean expression using basic gates and simplify same.

$$y = AB + BC (B+C)$$
 - b) Design 4 bit binary to gray code converter. Using truth table.
 - c) Realize given expression using K-map

$$f(A, B, C, D) = \sum m(3, 5, 7, 8, 10, 11, 12, 13)$$
 - d) Draw JK master slave flip flop and explain its operations.
 - e) Calculate analog o/p of 4 bit DAC for digital input is 1100.
 Assume $V_{FS} = 5V$

5. Attempt any TWO of the following:**12**

- a) Draw and explain operation 4 bit universal shift register. Draw necessary waveforms.
- b) Draw block diagram of Dual slope ADC and explain its working.
- c) Subtract following using Two's complement method.
 $(15)_{10} - (32)_{10}$

6. Attempt any TWO of the following:**12**

- a) Design MOD-12 ripple counter. Write its truth table with waveform.
 - b) Design 16:1 MUX using 4:1 MUX.
 - c) Compare TTL and CMOS with following points.
 - (i) Fan IN
 - (ii) FAN OUT
 - (iii) Propagation delay
 - (iv) Power dissipation
-