

22323

21222

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

15 minutes extra for each hour

- Instructions* – (1) All Questions are *Compulsory*.
- (2) Answer each next main Question on a new page.
- (3) Illustrate your answers with neat sketches wherever necessary.
- (4) Figures to the right indicate full marks.
- (5) Assume suitable data, if necessary.
- (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

1. **Attempt any FIVE of the following:** **10**
- a) Define term 2'S complement.
- b) State the necessity of Multiplexer.
- c) List the types of triggering.
- d) List any four features of 8086 microprocessor.
- e) Convert  $(85.63)_{10}$  to binary number.
- f) State the functions of following pins of 8086 microprocessor.
- i) ALE
- ii)  $DT/\bar{R}$
- iii)  $M/\bar{I}_o$
- iv) HOLD
- g) State the function of STC and AAA instructions of 8086 microprocessor.

P.T.O.

- 2. Attempt any THREE of the following:** **12**
- a) Explain with Justification NAND gate as a Universal gate.
  - b) With reference to K-MAP explain
    - i) Disallowed group
    - ii) Quad
    - iii) Octet
    - iv) Overlapping group
  - c) Explain J-K flip flop with the help of neat diagram. Write its truth table.
  - d) With the help of boolean laws prove  
 $(A + \bar{B} + AB) (A + B) \bar{A} \cdot \bar{B} = 0$
- 3. Attempt any THREE of the following:** **12**
- a) Convert following decimal number in BCD code an Excess-3 code.
    - i)  $(48)_{10}$
    - ii)  $(222)_{10}$
  - b) Compare the following terms
    - i) RCR and RCL
    - ii) JUMP and CALL
  - c) Explain S-R flip flop using NOR gate. Write truth table.
  - d) Design half subtractor using logic gates. Write truth table.
- 4. Attempt any THREE of the following:** **12**
- a) Explain Addressing modes of 8086 microprocessor.
  - b) Design 4:1 Multiplexer using NAND gates only.
  - c) Compare sequential logic circuit and combinational logic circuit.
  - d) Explain concept of pipelining with neat diagram.
  - e) Explain Min term and Max term in detail with suitable example.

5. Attempt any TWO of the following:

12

- Describe the operation performed by instruction IMUL and AAM.
- Draw output waveform at point A and at point B for the circuit shown in given Figure No. 1.

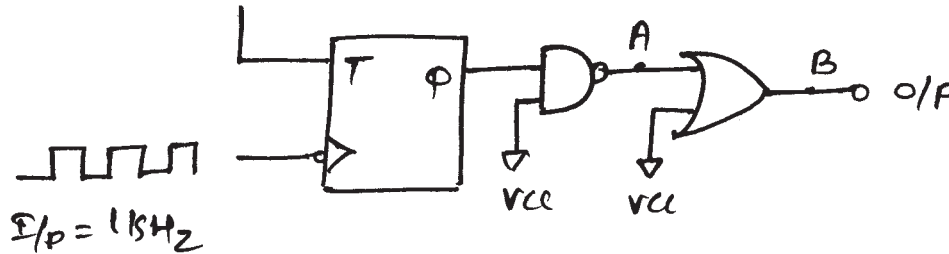


Fig. No. 1.

- Draw flag register format of 8086 microprocessor. Explain TF, DF, IF, CF flag registers.

6. Attempt any TWO of the following:

12

- Describe physical address generation steps with suitable example.
- Design T. flip flop using J-K flip flop. Write its truth table.
- Identify the addressing modes used in following instructions
  - MOV DS, AX
  - MOV AX, [4172H]
  - MUL AL, BL
  - ADD AX, [SI]
  - ADD AX [SI] BX [04]
  - INC [4712H]