

22324

21819

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.

Marks

1. **Attempt any FIVE of the following :** **10**
 - (a) Draw power triangle for R-C series circuit. State the nature of power factor of this circuit.
 - (b) Draw a phasor diagram for series R-L circuit showing supply voltage V , supply current I , voltage across resistor V_R & voltage across inductor V_L .
 - (c) What is current magnification in parallel R-L-C circuit.
 - (d) Define : Phase sequence and write equations for instantaneous values of 3-ph voltages.
 - (e) Distinguish clearly between loop and mesh.
 - (f) State Thevenin's theorem.
 - (g) State Reciprocity theorem.

2. **Attempt any THREE of the following :** **12**
 - (a) An AC series circuit consisting of $R = 15 \Omega$, $L = 0.1 \text{ H}$ and $C = 80 \mu\text{F}$ is supplied from 230 V, 50 Hz power supply. Determine :
 - (i) Impedance of circuit
 - (ii) Current drawn by the circuit
 - (iii) Circuit power factor
 - (iv) Reactive power drawn by circuit

[1 of 4]

P.T.O.

- (b) An AC circuit consists of two branches in parallel.
 Branch I : $R = 10 \Omega$ and $L = 0.1 \text{ H}$ in series.
 Branch II : $C = 50 \mu\text{F}$.
 If the circuit is supplied from 200 V, 50 Hz supply, determine :
- Branch impedances.
 - Branch currents
 - Circuit power factor
 - Power consumed by the circuit
- (c) A star connected 3-ph load is supplied from 3-ph, 415 V, 50 Hz supply. If the line current is 20 A and total power taken from supply is 10 kW, then determine :
- Load resistance and reactance per phase.
 - Load power factor
 - Total 3-phase reactive power
- (d) Using Node analysis, find current I in the circuit shown in Fig. No. 1.

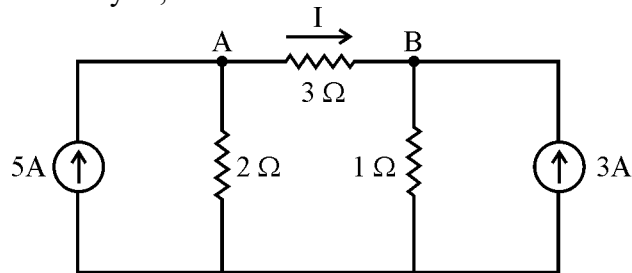


Fig. No. 1

3. Attempt any THREE of the following :

12

- A series R-L-C circuit consists of $R = 15 \Omega$, $L = 0.5 \text{ H}$ and $C = 25 \mu\text{F}$. If the circuit is supplied from 230 V, 50 Hz AC supply, determine :
 - Circuit power factor
 - Active power
 - Reactive power
 - Apparent power
- Two parallel impedances $Z_1 = (10 + j8) \Omega$ and $Z_2 = (15 - j10) \Omega$ are connected to 230 V, 50 Hz AC supply. Using admittance method, calculate branch currents, total current and power factor of whole circuit.
- Explain 'Neutral Shift' in case of 3-phase star-connected unbalanced load.
- With neat circuit diagram, explain how to convert voltage source into current source and vice-versa.

- (e) Using Mesh analysis, find current I in the circuit shown in Fig. No. 2.

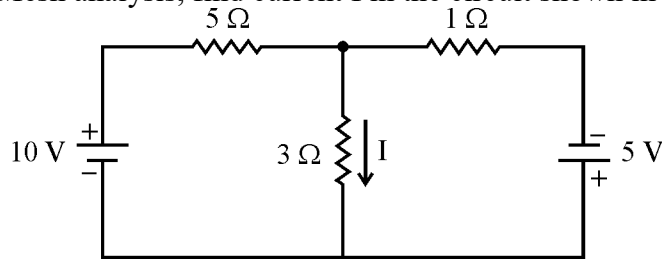


Fig. No. 2

4. Attempt any THREE of the following :

12

- (a) An inductive coil having resistance of $5\ \Omega$ and inductance of $0.2\ \text{H}$ is connected in series with a capacitor of $20\ \mu\text{F}$. If this combination is connected to $230\ \text{V}$, variable frequency supply, determine :
- Resonant Frequency
 - Quality factor
 - Current at resonance
 - Voltage across inductive coil at resonance
- (b) A coil having resistance of $10\ \Omega$ and inductance of $0.15\ \text{H}$ is connected in parallel with R-C series combination having $R = 5\ \Omega$ & $C = 20\ \mu\text{F}$. If supply voltage is $110\ \text{V}$, $50\ \text{Hz}$, then
- Draw circuit diagram
 - Calculate branch currents using impedance method
 - Power absorbed by the coil
- (c) Three equal impedances having $R = 20\ \Omega$ in series with $C = 50\ \mu\text{F}$, are connected in delta across $415\ \text{V}$, 3-ph, $50\ \text{Hz}$ AC supply. Determine :
- Impedance per phase
 - Phase and line currents
 - Total 3-ph power consumed by load
- (d) With neat circuit diagram, explain the concept of duality in Electric circuit. State any four examples (pairs) of duality in electric circuit.

5. Attempt any TWO of the following :

12

- (a) An inductive coil having resistance of $10\ \Omega$ and inductance of $0.5\ \text{H}$ is connected in parallel with a capacitor of $50\ \mu\text{F}$. Determine :
- Parallel resonant frequency
 - Quality factor of parallel circuit
 - Power consumed by circuit at resonance, if the supply voltage is $230\ \text{V}$.

P.T.O.

- (b) Reduce the network shown in Fig. No. 3 by applying Star/Delta or Delta/Star transformation and determine equivalent resistance R_{AB} .

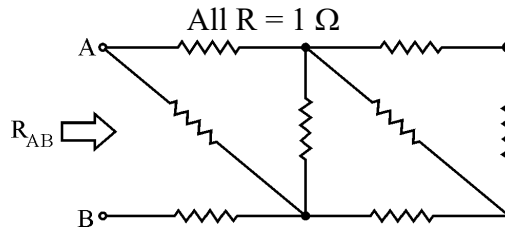


Fig. No. 3

- (c) For network shown in Fig. No. 4, determine value of R so that maximum power is delivered to it. Also compute the maximum power delivered.

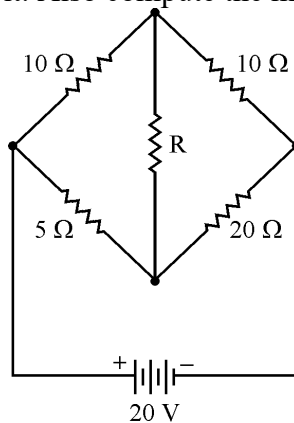


Fig. No. 4

6. Attempt any TWO of the following :

12

- (a) A series RLC circuit consists of $R = 10 \Omega$, $L = 0.5 \text{ H}$ and $C = 20 \mu\text{F}$, is connected to 230 V, variable frequency supply. Determine :
- Resonant frequency
 - Voltage magnification
 - Current drawn by circuit
 - Voltage across each element
 - Power factor at resonance
 - The power consumed at resonance
- (b) Draw complete phasor diagram of voltages & currents for balanced delta-connected load, and prove the relationship between :
- Line current & phase current
 - Line voltage & phase voltage
- (c) Apply superposition theorem to compute current I in the network shown in Fig. No. 5.

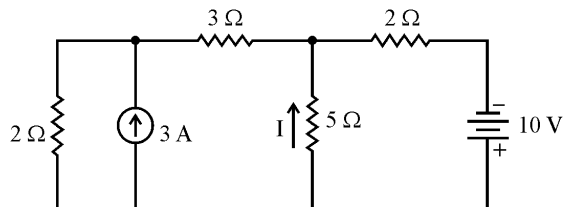


Fig. No. 5