

22324

11920

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following : 10
- (a) Define Conductance and Susceptance related to AC circuit and state their units.
 - (b) Draw power triangle for R-L series circuit. Write equation of power in rectangular form.
 - (c) Express an instantaneous value of an alternating current varying sinusoidally in terms of its maximum value, frequency and time.
 - (d) State relationship between line and phase values of voltage and current in balanced delta connection.
 - (e) Distinguish clearly between loop and mesh.
 - (f) State the value of internal resistance of (i) Ideal Voltage Source and (ii) Ideal Current Source.
 - (g) State Norton's Theorem.

[1 of 4]

P.T.O.

- 2. Attempt any THREE of the following : 12**
- (a) With neat diagram, explain the phasor representation of sinusoidal quantity.
 - (b) For a parallel circuit consisting of an inductive branch (RL) in parallel with a capacitive branch (RC), draw phasor diagram and derive equation for resonant frequency.
 - (c) With the help of neat phasor diagram, derive the relationship between line and phase values of voltage in balanced star connection.
 - (d) State the equivalent delta connection for star connection of three resistances R_1 , R_2 & R_3 , with proper equations.
- 3. Attempt any THREE of the following : 12**
- (a) For series R-L-C circuit, draw neat circuit diagram. State the conditions for RLC series ckt. Draw phasor diagram and voltage triangle impedance triangle for any 1 condition.
 - (b) State any four properties of Parallel Resonance.
 - (c) With neat labelled diagram, explain unbalanced star connected load.
 - (d) With neat circuit diagram, explain how to convert a practical voltage source into an equivalent practical current source.
 - (e) Explain the concept of “duality” in electric circuit with one example.
- 4. Attempt any THREE of the following : 12**
- (a) A series R-L-C circuit has $R = 5\Omega$, $L = 10 \text{ mH}$ and $C = 15 \mu\text{F}$. Calculate :
 - (i) Resonant frequency
 - (ii) Q-factor of the circuit
 - (iii) Bandwidth
 - (iv) Voltage magnification.
 - (b) Explain the “Current Magnification” in parallel resonant circuit consisting of inductive branch (RL) in parallel with a pure capacitor (C). Derive equation for it.

- (c) Draw waveform of three-phase voltages. Draw phasor diagram for these voltages. Write equations for instantaneous values of these voltages. Express these voltages in polar form.
- (d) State and explain "Reciprocity theorem".

5. Attempt any TWO of the following :

12

- (a) A coil having resistance of 5Ω and an inductance of 0.2 H is connected in parallel with a series combination of 10Ω resistor and $80 \mu\text{F}$ capacitor. If supply voltage is 230 V , 50 Hz , determine :
- Total circuit impedance.
 - Total current taken by the circuit.
 - Power factor of the circuit.
 - Branch currents.
 - Power consumed by the circuit.
- (b) Using mesh analysis, find current in 5Ω resistor in the network shown in Fig. 5(b).

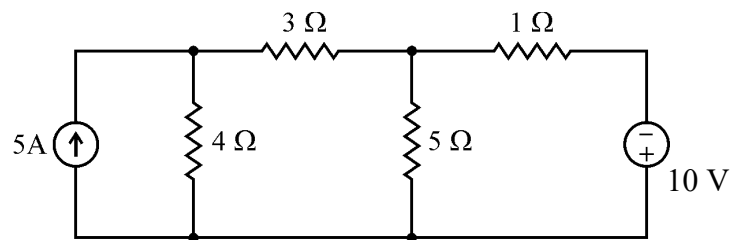


Fig. No. 5 (b)

- (c) Find the current in 5Ω resistor in the network shown in Fig. 5(c) by using Thevenin's theorem.

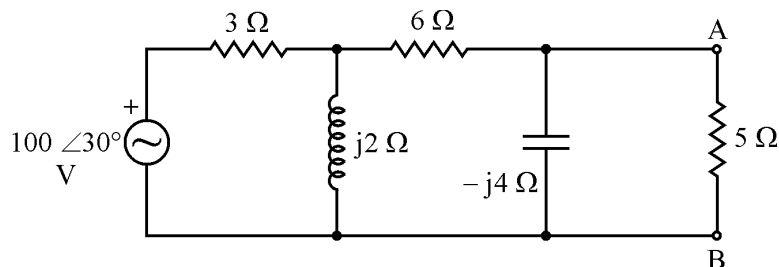


Fig. No. 5 (c)

6. Attempt any TWO of the following :

12

- (a) For a series R-L-C circuit consisting of $R = 5 \Omega$, $L = 0.01 \text{ H}$ and $C = 10 \mu\text{F}$ supplied with 230 V, 50 Hz supply, determine :
- Circuit impedance
 - Circuit current
 - Circuit power factor
 - Active power
 - Reactive power
 - Apparent power
- (b) A star connected capacitive load is supplied from 3 ϕ , 415 V, 50 Hz supply. If the line current is 15 A and total 3 ϕ power taken from supply is 30 kW , find :
- Power factor
 - Resistance in each phase
 - Capacitance in each phase.
- (c) Determine the voltage 'V' across 5Ω resistor in network shown in Fig. 6(c) using superposition theorem.

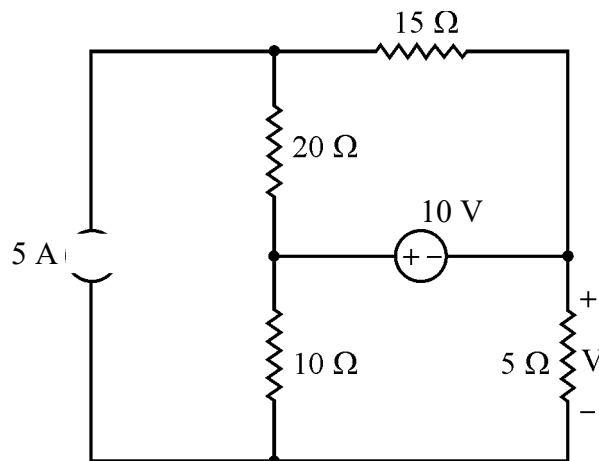


Fig. No. 6 (c)