



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code: **22330**

1

Important Instructions to examiners:

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more importance (Not applicable for subject English and Communication Skills).
- 4) While assessing figures, examiner may give credit for principal components indicated in the figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case of some questions credit may be given by judgement on part of examiner of relevant answer based on candidate's understanding.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

Q. No.	Sub Q. N.	Answers	Marking Scheme
1	(A)	Attempt any FIVE of the following :	10- Total Marks
	(a)	Define impedance and reactance related to single phase AC series circuit. Give unit of both.	2M
	Ans:	Impedance of single phase AC series circuit is defined as the net opposition offered to the flow of AC current by the combination of R, L and C. Unit of Impedance is Ω (Ohm). Reactance of single phase AC series circuit is defined as the opposition offered to the flow of AC current by either inductor(L) or capacitor(C). Unit of reactance is Ω (Ohm).	Each correct definition with its unit- 1M
	(b)	Draw the impedance triangle for R-L series circuit.	2M


SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

2
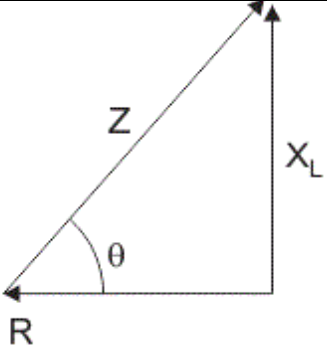
<p>Ans:</p>	 <p>Fig. impedance triangle for R-L series circuit.</p>	<p>impedance triangle-2M</p>
<p>(c)</p>	<p>State Q factor for parallel R.L.C. circuit.</p>	<p>2M</p>
<p>Ans:</p>	<p>Q factor for parallel R.L.C. circuit is defined as the current magnification provided at resonance. The magnitude of current flowing through inductor and capacitor is equal to Q times the input sinusoidal current I.</p> <p>As the parallel circuit magnifies the current it is also called as the current resonance circuit.</p> <p>OR</p> <p>The Quality factor of Parallel resonance RLC circuit is defined as the ratio of current circulating between its two branches to the line current drawn from the supply.</p> <p>Mathematically, $Q = R X_c$</p>	<p>Any correct definition-2M</p>
<p>(d)</p>	<p>Give four steps to solve nodal analysis.</p>	<p>2M</p>
<p>Ans:</p>	<p>four steps to solve nodal analysis-</p> <ol style="list-style-type: none"> 1.all the nodes present in the network including the reference(ground) node)are identified and marked . The number of equations to be solved is given by (n-1) where n= no of independent nodes. 2. Mark all the branch currents. 3. Using KCL write current equation for each node in terms of node voltage and sources present. 4. The equations can be solved either simultaneously or by Cramer's rule to obtain various node voltages. 	<p>Each step - 1/2 M</p>

SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code: 22330

	The current flowing through any element can be found out by substituting the value of node voltages in the relevant equation.	
e)	Write the formula for star to delta.	2M
Ans:	<p>The formula for star to delta</p> <p><u>Star to Delta (Y to Δ) Resistance Conversion Formula</u></p> $R_a = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$ $R_b = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$ $R_c = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$	Correct formulae with diagram- 2M
f)	State Thevenin's theorem.	2M
Ans:	Any network containing active and/or passive elements and one or more dependent and/or independent voltage/or current sources can be replaced by an equivalent network containing a voltage source (Thevenin's equivalent voltage V_{TH} or V_{OC}) and a series resistance (called Thevenin's equivalent resistance R_{TH}) where V_{TH} is the voltage measured across open terminals A and B and R_{th} is the resistance across same terminals A and B when all the sources are replaced by their internal resistances.	Statement (2 Mark)
g)	State the significance of two port network.	2M
Ans:	The significance of two port network-	2M

SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network


Model Answer

Subject Code: 22330

Any electrical network can be easily analyzed if it is represented with an equivalent model, which gives the relation between input and output variables. A two port network is a network having 2 ports. One port is used as input port and the other port is used as output port. These ports are called port1 and port2 respectively.

Once a network is represented in this equivalent form, the response of the network to signals applied to the ports can be calculated easily, without solving for all the internal voltages and currents in the network. It also allows similar circuits or devices to be compared easily.

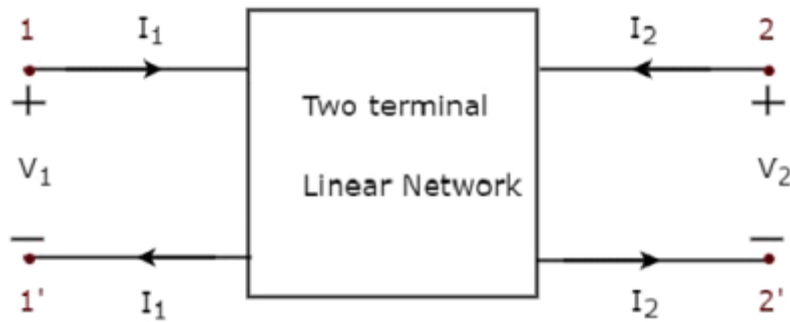A two port network representation is shown in the following figure.



Here, terminals 1 and 1' represent port1 and terminals 2 & 2' represent port2.

The common models that are used are referred to as z-parameters, y-parameters, h-parameters, g-parameters, and ABCD-parameters..

Q. No.	Sub Q. N.	Answers	Marking Scheme
2		Attempt any THREE of the following:	12- Total Marks
	a)	An RC series circuit consists of $R = 10\Omega$ and $C = 200 \mu\text{f}$.it is connected across 250 V, 50Hz, 1 ϕ AC. Calculate the value of power consumed by the circuit.	4M
	Ans:		1M -Xc, 1M-Z,




SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

5


	<p>Solution -:</p> <p>Given -:</p> $R = 10\Omega, C = 200\mu F, V = 250V, f = 50\text{ Hz}$ <p>Capacitive Reactance, X_C :-</p> $X_C = \frac{1}{2\pi fC}$ $= \frac{1}{2 \times \pi \times 50 \times 200 \times 10^{-6}}$ $\therefore X_C = 15.91\Omega$ <p>\therefore Impedance Z :-</p> $\therefore Z = \sqrt{R^2 + X_C^2} = \sqrt{10^2 + (15.91)^2}$ $\therefore Z = 18.79\Omega$ <p>Now, the total current I :</p> $\therefore I = \frac{V}{Z} = \frac{250}{18.79} = 13.30\text{ A}$ <p>Power Factor, $\cos \phi = \frac{R}{Z} = \frac{10}{18.79}$</p> $\therefore \text{P.F.} = \cos \phi = 0.53 \text{ (leading)}$ <p>And, the value of Power consumed by the circuit is P:-</p> $P = V \cdot I \cos \phi$ $= 250 \times 13.30 \times 0.53$ $\therefore P = 1762.25 \text{ watt}$ <p>OR $\therefore P = 1.7622 \text{ Kwatt}$</p> <p> Scanned with CamScanner</p>	<p>1M- Power Factor, 1M- Power consumed</p>
<p>b)</p>	<p>Describe the procedure to tune the given electrical circuit using the principles of resonance.</p>	<p>4M</p>
<p>Ans:</p>	<p>An electrical circuit can be tuned to resonant frequency in any one of the following ways:</p>	<p>4M</p>

SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code: 22330

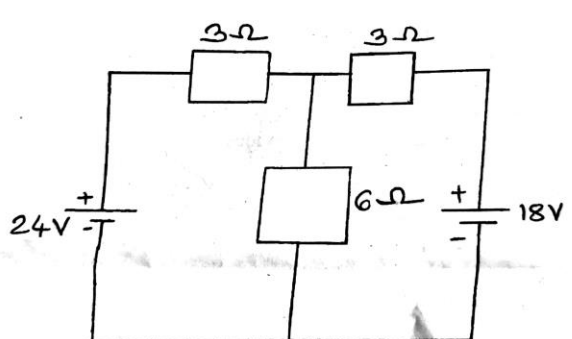	<p>i) If the circuit parameters like resistance, inductance and capacitance are of fixed value, the resonant frequency is calculated. Then by connecting a function generator, the input frequency can be varied till the circuit is tuned to the desired resonant frequency.</p> <p>ii) If the circuit is to be tuned to a particular frequency, and the frequency of the supply cannot be varied, then by using either a variable capacitor or variable inductor, the variable element can be varied till the circuit is tuned to the desired resonant frequency.</p>	
c)	<p>Find the current in 6Ω resistor in the circuit shown in Fig. No. 1 using mesh analysis.</p>  <p style="text-align: center;"><u>Fig. No. 1</u></p>	4M

SUMMER-19 EXAMINATION

Subject Name: Electric circuits and network


Model Answer

Subject Code 22330

7

Ans:

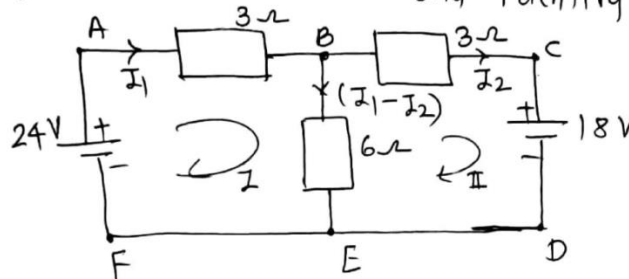Step 1 :- Name the nodes and identify the loops :-



Step 2 :- Equation for loop I (A B E F A) :-

Apply KVL,

$$24 - 3I_1 - 6(I_1 - I_2) = 0$$

$$-3I_1 - 6I_1 + 6I_2 = -24$$

$$-9I_1 + 6I_2 = -24$$

$$\therefore 9I_1 - 6I_2 = 24 \quad \text{--- (1)}$$

Step 3 :- Equation for loop II (B C D E B) :-

$$-3I_2 - 18 - 6(I_2 - I_1) = 0$$

$$-3I_2 - 6I_2 + 6I_1 = 18$$

$$6I_1 - 9I_2 = 18 \quad \text{--- (2)}$$

Solving equation (1) and (2) by Determinant Method

$$D = \begin{vmatrix} 9 & -6 \\ 6 & -9 \end{vmatrix} = (-9) \times 9 - [(-6) \times 6]$$

$$= -81 + 36$$

$$\therefore D = -45$$

$$D_1 = \begin{bmatrix} 24 & -6 \\ 18 & -9 \end{bmatrix} = 24 \times (-9) - [(-6) \times 18]$$

$$= -216 + 108$$

$$\therefore D_1 = -108$$

$$D_2 = \begin{bmatrix} 9 & 24 \\ 6 & 18 \end{bmatrix} = 9 \times 18 - (24 \times 6)$$

$$= 162 - 144$$

$$\therefore D_2 = 18$$

$$\therefore I_1 = \frac{D_1}{D} = \frac{-108}{-45} = 2.4 \text{ A}$$

$$I_2 = \frac{D_2}{D} = \frac{18}{-45} = -0.4 \text{ A}$$

$$\therefore \text{The current in } 6\Omega \text{ resistor is } (I_1 - I_2)$$

$$= 2.4 - (-0.4)$$

$$= 2.8 \text{ A}$$

½ M-
each
equation

1M for
I₁,

1M for
I₂,

1M for
current
through
6 ohm
resistor



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code **22330**

- d) Find the value of R_L so that maximum power will transfer from source to it . also write equation for P_{MAX} (Fig. No. 2)

4M

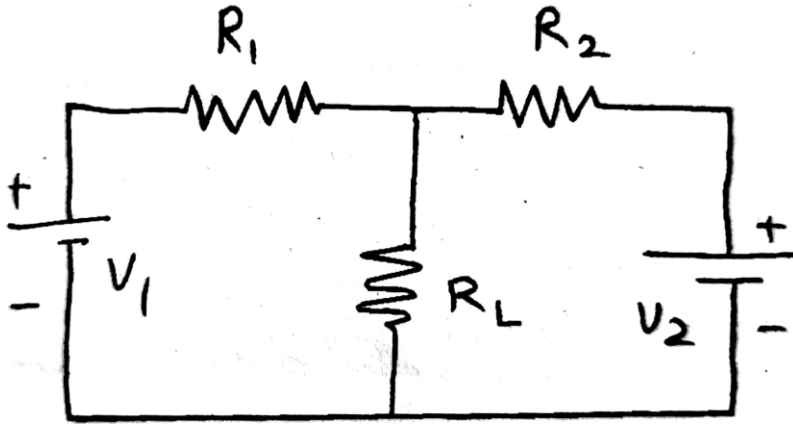


Fig. No. 2




SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330
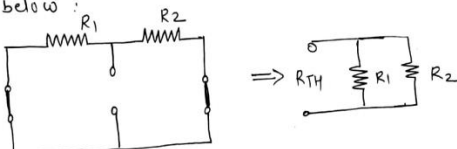
<p>Ans:</p>	<p>Replace the voltage sources V_1 and V_2 by short circuit to obtain the circuit shown below :</p>  <p>$\therefore R_{TH} = R_1 \parallel R_2$ $\therefore R_{TH} = \frac{R_1 \times R_2}{R_1 + R_2}$</p> <p>But the condition for maximum power transfer to the load is - $R_L = R_{TH}$.</p> <p>\therefore The value of $R_L = R_{TH}$ so that maximum power will transfer from source to it.</p> <p>The equation for P_{max} -</p> $P_{L(max)} = \left(\frac{V_{TH}}{R_{TH} + R_{TH}} \right)^2 R_{TH}$ <p>Substitute $R_L = R_{TH}$</p> <p>\therefore Therefore the power transfer to the load is given by the equation</p> $P_L = \frac{V_{TH}^2}{4 R_{TH}}$	<p>3M-for R_L 1M for power formula</p>	
<p>Q. No.</p>	<p>Sub Q. N.</p>	<p>Answers</p>	<p>Marking Scheme</p>
<p>3</p>	<p>Attempt any THREE of the following :</p>		<p>12- Total Marks</p>
	<p>a)</p>	<p>List the power factor improves technique and explain any one with advantage and disadvantage</p>	<p>4M</p>
	<p>Ans:</p>	<p>Power factor improvement techniques are</p> <ul style="list-style-type: none"> i) Synchronous Motors (or capacitors) ii) Static Capacitors 	<p>2Marks for Listing Techniques</p>



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

10

		<p>iii) Phase Advancers</p> <p>i) Synchronous Motors (or capacitors) : These machines draw leading kVAR when they are over-excited and, especially, when they are running idle. They are employed for correcting the power factor in bulk and have the special advantage that the amount of correction can be varied by changing their excitation.</p> <p>ii) Static Capacitors : They are installed to improve the power factor of a group of a.c. motors and are practically loss-free (i.e. they draw a current leading in phase by 90°). Since their capacitance is not variable, they tend to over-compensate on light loads, unless arrangements for automatic switching of the capacitor bank are made.</p> <p>iii) Phase Advancers : They are fitted with individual machines. However, it may be noted that the economical degree of correction to be applied in each case, depends upon the tariff arrangement between the consumers and the supply authorities.</p>	<p>2Marks for any one technique</p>																
	b)	<p>Compare series resonance to parallel resonance on the basis of:</p> <p>(i) Resonant frequency (ii) Impedance (iii) Current and (iv) Magnification.</p>	<p>4M</p>																
	Ans:	<table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 10%;">S.No.</th> <th style="width: 25%;">Parameter</th> <th style="width: 30%;">Series Circuit</th> <th style="width: 35%;">Parallel Circuit</th> </tr> </thead> <tbody> <tr> <td style="text-align: center;">1</td> <td>Resonant frequency</td> <td style="text-align: center;">$f_r = \frac{1}{2\pi\sqrt{LC}}$</td> <td style="text-align: center;">$f_r = \frac{1}{2\pi\sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}}$</td> </tr> <tr> <td style="text-align: center;">2</td> <td>Impedance</td> <td>Minimum, Z = R</td> <td>Maximum, Z = L/CR</td> </tr> <tr> <td style="text-align: center;">3</td> <td>Current</td> <td>Maximum, I = V/R</td> <td>Minimum, I = V/(L/CR)</td> </tr> </tbody> </table>	S.No.	Parameter	Series Circuit	Parallel Circuit	1	Resonant frequency	$f_r = \frac{1}{2\pi\sqrt{LC}}$	$f_r = \frac{1}{2\pi\sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}}$	2	Impedance	Minimum, Z = R	Maximum, Z = L/CR	3	Current	Maximum, I = V/R	Minimum, I = V/(L/CR)	<p>1 marks for each point</p>
S.No.	Parameter	Series Circuit	Parallel Circuit																
1	Resonant frequency	$f_r = \frac{1}{2\pi\sqrt{LC}}$	$f_r = \frac{1}{2\pi\sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}}$																
2	Impedance	Minimum, Z = R	Maximum, Z = L/CR																
3	Current	Maximum, I = V/R	Minimum, I = V/(L/CR)																

SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

	4	Magnification	Voltage magnification takes place	Current magnification takes place	
c)		Write the procedure to convert voltage source into equivalent current source. Give its application. Draw neat diagrams of both the sources.			4M
Ans:		<p>A voltage source with a series resistance can be converted into (or replaced by) and equivalent current source with a parallel resistance.</p> <p>The steps for converting practical voltage source into practical current source.</p> <p>i) Find the value of current supplied by the source when a 'short' is put across terminals A and B.</p> <p>Therefore,</p> <p style="text-align: center;">$\text{Current } I = V/R$</p> <p>ii) The value of resistance which is connected in parallel with the equivalent current source have the same value of series resistance ($R_s = R_{sh}$).</p> <p>ii) This equivalent current source is then connected in parallel with the shunt (parallel) resistance.</p> <div style="text-align: center; margin-top: 20px;"> </div>			<p>2 marks for Procedu re</p> <p style="text-align: right; margin-top: 20px;">1 mark for diagram</p>


SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

12

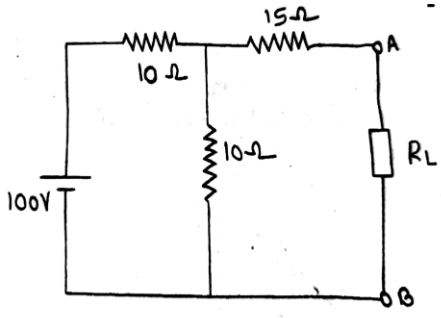	<p>Application : For the simplification and analysis of complex networks the transformation of voltage source to an equivalent current source or vice versa is often necessary.</p>	<p>1 mark for Application</p>
<p>d)</p>	<p>Find Norton's equivalent circuit of the Fig. shown (Fig. No. 3)</p> <div data-bbox="617 693 1055 1008" data-label="Diagram"></div> <p style="text-align: center;"><u>Fig. No. 3</u></p>	<p>4M</p>
<p>Ans:</p>		


SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

13

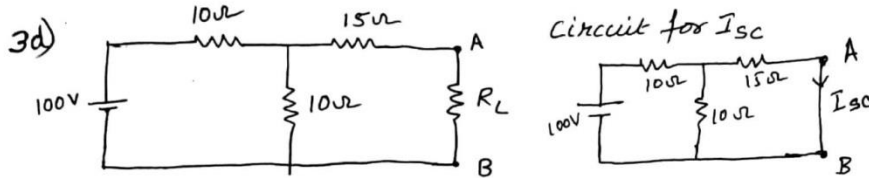

Step 1: To obtain the value of I_{sc} :

The Total resistance R_T is given by

$$R_T = 10 + [10 \parallel 15]$$

$$= 10 + \left[\frac{10 \times 15}{10 + 15} \right]$$

$$= 10 + 6 = 16 \Omega$$

The Source current I is given by


$$I = \frac{V}{R_T} = \frac{100}{16} = 6.25 \text{ A}$$

The short circuit current I_{sc} is the current flowing through the 15Ω resistor

$$\therefore I_{sc} = I \times \frac{10}{10 + 15} = 6.25 \times \frac{10}{25}$$

$$I_{sc} = 2.5 \text{ A}$$


Step 2: To obtain the value of R_{th}

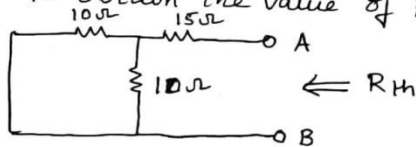

$$\therefore R_{th} = 15 + [10 \parallel 10]$$

$$= 15 + 5 = 20 \Omega$$

Step 3: Norton's equivalent circuit

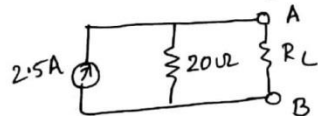

2marks for obtaining Short circuit current

1mark for R_{th}

1mark for equivalent circuit



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

14

Q. No.	Sub Q. N.	Answers	Marking Scheme
4		Attempt any THREE of the following :	12- Total Marks
	(a)	<p>In a series circuit containing pure resistance pure inductance, the current and voltage are expressed as:</p> <p>$I(t) = 5 \sin (314t + 2 \pi/3)$ and $v(t) = 20 \sin (314t + 5 \pi/6)$</p> <p>Find:</p> <ul style="list-style-type: none"> (i) Impedance of circuit (ii) Resistance of circuit (iii) Inductance in circuit (iv) Average power drawn by circuit. 	4M
	Ans:	<p>$I(t) = 5 \sin (314t + 2 \pi/3)$ and $v(t) = 20 \sin (314t + 5 \pi/6)$</p> <p>Converting the above standard sinusoidal forms into polar forms</p> <p>Rms values of current and voltage are</p> <p>$I = 5/\sqrt{2} = 3.54 \text{ A}$; $V = 20/\sqrt{2} = 14.14 \text{ V}$</p> <p>Converting the above standard sinusoidal forms into polar forms</p> <p>$\vec{I} = (3.54 \angle 120^\circ) \text{ A}$</p> <p>$\vec{V} = (14.14 \angle 150^\circ) \text{ V}$</p> <p>By Ohm's law,</p> <p>Circuit Impedance, $\vec{Z} = \vec{V} / \vec{I} = (14.14 \angle 150^\circ) / (3.54 \angle 120^\circ)$</p> <p style="text-align: center;">$= (4 \angle 30^\circ) \Omega$</p>	1 mark for Impedance



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

15

		<p style="text-align: center;">$= (3.46 + j2) \Omega$</p> <p>From polar form of Impedance</p> <p>i) Impedance of circuit = $Z = 4 \Omega$</p> <p>From Rectangular form of impedance</p> <p>ii) Resistance of circuit $R = Z \cos\phi = 4 \cos(30) = 3.46 \Omega$</p> <p>iii) Inductance of circuit L</p> <p style="padding-left: 40px;">we know that $X_L = 2 \Omega$ (from rectangular form of impedance)</p> <p style="text-align: center;">$X_L = 2\pi fL$</p> <p style="text-align: center;">$L = X_L / 2\pi f = 2 / (2\pi \times 50) = 6.37 \times 10^{-3} \text{ H}$</p> <p>From polar form of Impedance , $\phi = 30^\circ$</p> <p>So, $\text{pf} = \cos\phi$</p> <p style="padding-left: 40px;">$= \cos 30^\circ$</p> <p style="padding-left: 40px;">$= 0.866$ lagging</p> <p>iv) Average power, $P = VI \cos\phi$</p> <p style="padding-left: 40px;">$= 14.14 \times 3.54 \times \cos 30^\circ$</p> <p style="padding-left: 40px;">$= 43.35 \text{ W}$</p>	<p>1 mark for Resistance</p> <p>1 mark for Inductance</p> <p>1 mark for Average power</p>
	(b)	Find I, I_1, I_2 power factor of the circuit in Fig. No. 4	4M

SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

16

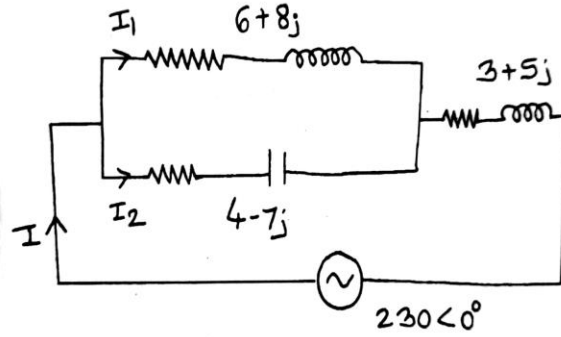


Fig. No. 4


Ans:

SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

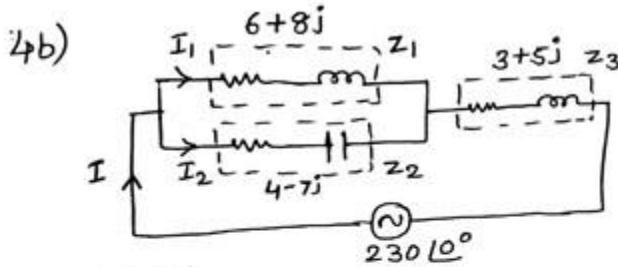

sol Given: $Z_1 = 6 + 8j$, $Z_2 = 4 - 7j$, $Z_3 = 3 + 5j$, $V = 230 \angle 0^\circ$

Total Impedance

$$Z = (Z_1 \parallel Z_2) + Z_3 = \frac{Z_1 Z_2}{Z_1 + Z_2} + Z_3$$

But $Z_1 + Z_2 = 6 + 8j + 4 - 7j$
 $= 10 + j$
 $= 10 \angle 5.71^\circ$

Polar form of $Z_1 = (10 \angle 53.13)$

" " $Z_2 = (8.06 \angle -60.25)$

$$\therefore \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{(10 \angle 53.13) \times (8.06 \angle -60.25)}{10 \angle 5.71}$$

$$= \frac{80.6 \angle -7.12}{10 \angle 5.71} = 8.06 \angle -12.83^\circ$$

$$= 7.85 - 1.78j$$

$$\therefore Z = 7.85 - 1.78j + 3 + 5j$$

$$= 10.85 + 3.22j$$

$$= 11.31 \angle 16.52^\circ$$

• Total current $I = \frac{V}{Z} = \frac{230 \angle 0}{11.31 \angle 16.52}$

$$\therefore I = 20.33 \angle -16.52^\circ \text{ A}$$

• $I_1 = I \times \frac{Z_2}{Z_1 + Z_2} = (20.33 \angle -16.52) \frac{8.06 \angle -60.25}{10 \angle 5.71}$

$$= (20.33 \angle -16.52) (0.806 \angle -65.96)$$

$$I_1 = 16.38 \angle -82.48^\circ \text{ A}$$

1mark
for I

1mark
for I₁

1mark
for I₂

1mark
for
Power
factor

SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

18

$$\begin{aligned}
 \bullet I_2 &= I \times \frac{Z_1}{Z_1 + Z_2} = (20.33 \angle -16.52^\circ) \frac{(10 \angle 53.13^\circ)}{(10 \angle 5.71^\circ)} \\
 &= (20.33 \angle -16.52^\circ) (1 \angle 47.42^\circ) \\
 \therefore I_2 &= \underline{20.33 \angle 30.9^\circ \text{ A}}
 \end{aligned}$$

$$\begin{aligned}
 \bullet \text{ power factor} &= \cos \phi = \cos (-16.52^\circ) \\
 &= \underline{0.958 \text{ lagging}}
 \end{aligned}$$


(c) Explain the term bandwidth of a series resonant circuit. Derive its equation.

4M

Ans: Band width (BW) of a series resonance circuit is defined as the range of frequency over which circuit current is equal to or greater than $\frac{I_r}{\sqrt{2}}$ or 70.7 % of maximum current where I_0 or I_r = current at resonance.

Explanation 2 Marks

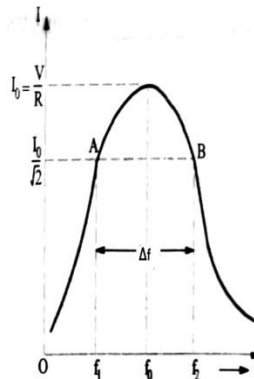The resonance curve for a series RLC circuit is shown below:



From the graph it is clear that for all frequencies lying between f_1 and f_2 the circuit current is equal to or greater than 70.7 % of maximum current i.e.



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code **22330**

19

$$I_r = V/R$$

Thus Band width of the circuit, $BW = \Delta f = (f_2 - f_1)$ Hz

$$\text{Or } BW = \Delta \omega = (\omega_2 - \omega_1) \text{ rad/sec}$$

Derivation of equation for bandwidth -

The relationship between bandwidth , Q factor and resonant frequency is given by

$$(f_2 - f_1) = f_r / Q_r$$

Where $f_2 - f_1 =$ bandwidth, $f_r =$ resonant frequency and $Q_r =$ Q factor at resonance

$$\text{But } f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$\text{And } Q_r = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Substituting these values in the equation for bandwidth,

$$\Delta f = f_r / Q_r = \frac{\frac{1}{2\pi\sqrt{LC}}}{\frac{1}{R}\sqrt{\frac{L}{C}}} = \frac{R\sqrt{C}}{2\pi\sqrt{CL^2}} = \frac{R}{2\pi L} \text{ Hz}$$

$$\text{Therefore bandwidth } \Delta f = f_2 - f_1 = \frac{R}{2\pi L} \text{ Hz}$$

OR

$$\Delta \omega = 2\pi \Delta f = \frac{R}{L} \text{ rad/sec}$$

2marks
for
Derivati
on


SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

20
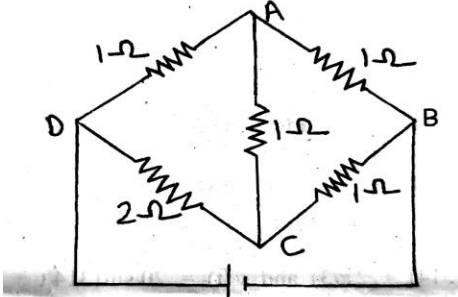
<p>(d)</p>	<p>A bridge network ABCD has arms AB, BC, CD and DA of resistances 1, 1, 2 and 1 ohm respectively . If the detector AC has a resistance of 1 ohm, determine by star/delta transformation, the network resistance as viewed from the battery terminals.</p> <div style="text-align: center;">  <p>Fig. No. 5</p> </div>	<p>4M</p>
<p>Ans:</p>		<p>2 marks for Converting delta to star</p> <p>2 marks for Network resistance</p>


SUMMER-19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

21

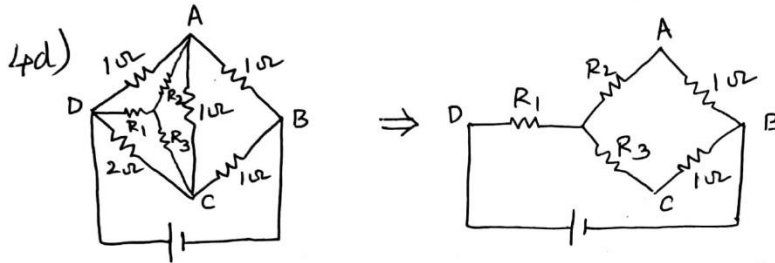


STEP 1: Converting the delta formed by ACD into equivalent star network.

(ie) $\Delta ACD \Rightarrow Y ACD$


$$\therefore R_1 = \frac{1 \times 2}{1+2+1} = \frac{2}{4} = 0.5 \Omega$$

$$R_2 = \frac{1 \times 1}{1+2+1} = \frac{1}{4} = 0.25 \Omega$$
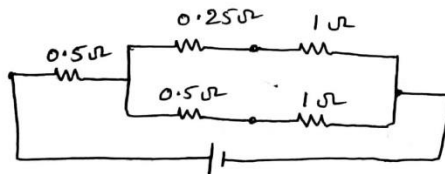
$$R_3 = \frac{1 \times 2}{1+2+1} = \frac{2}{4} = 0.5 \Omega$$



The above circuit is converted as

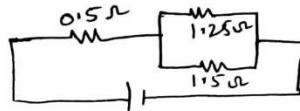

Here 1.25Ω & 1.5Ω are in parallel
 $[1.25 || 1.5] = 0.68$



\therefore network resistance = 1.18 Ω

Note: The problem can be done by converting delta ABC into equivalent star also.

(e) Find current through 6Ω resistor using superposition theorem. Fig. No. 6

4M



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

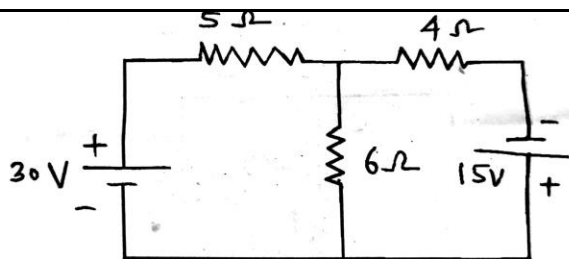


Fig. No. 6

Ans:

1mark
for R_T

SUMMER- 19 EXAMINATION


Subject Name: Electric circuits and network

Model Answer

Subject Code 22330


23

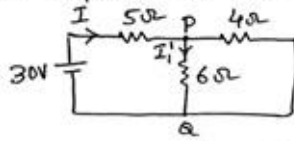4e) Replace the 15V source by a short circuit, keeping 30V



Resistor 6Ω & 4Ω are parallel
 $\therefore 6 \parallel 4 = 2.4\Omega$

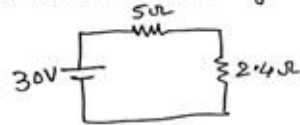→ Current through 6Ω Resistor due to 30V source is I'



Resistor 5Ω & 2.4Ω are in series

Total Resistance


$$R_T = 5 + 2.4 = 7.4\Omega$$

$$R_T = 7.4\Omega$$

$$\therefore \text{Total current } I = \frac{30}{7.4} = 4.05\text{A}$$


$$\therefore I' = I \times \frac{4}{4+6} = 4.05 \times \frac{4}{10} = \underline{1.62\text{A}}$$

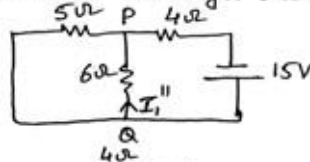→ Current through 6Ω Resistor due to 15V source is I''



Resistor 5Ω & 6Ω are in parallel

$$\therefore 5 \parallel 6 = \frac{30}{11} = 2.72\Omega$$

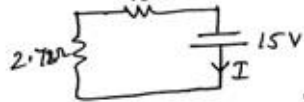

Resistor 2.72Ω & 4Ω are in series

\therefore Total Resistance is

$$R_T = 2.72 + 4 = 6.72\Omega$$

$$\therefore \text{Total current } I = \frac{V}{R_T} = \frac{15}{6.72} = 2.23\text{A}$$

$$\therefore I'' = I \times \frac{5}{5+6} = 2.23 \times \frac{5}{11}$$

$$I'' = -1.01\text{A} \quad (\text{As current is flowing from Q to P we will consider it to be negative})$$

\therefore Total current in 6Ω Resistor is (from P to Q)

$$I' + I''$$

$$= 1.62 - 1.01$$

$$I_{6\Omega} = 0.61\text{A}$$

1mark
for I'

1mark
for I''

1mark
for $I_{6\Omega}$



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code: **22330**

24

Q. No.	Sub Q. N.	Answers	Marking Scheme
5.		Attempt any TWO of the following:	12- Total Marks
	a)	A coil of resistance 20Ω and $200 \mu\text{H}$ is in parallel with a variable capacitor. The voltage of the supply is 20 V at a frequency of 10^6 Hz. Calculate : (i) The value of C to give resonance. (ii) The Q of the coil. (iii) The current in each branch of the circuit at resonance.	6M

SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

Ans:

Q. 59) Diagram \Rightarrow

Pg. No. ①

Dia 1 M

i) The value of 'C' to give resonance

* If value of 'R' is considered very small in comparison with inductor 'L' then

$$\therefore f_r = \frac{1}{2\pi\sqrt{LC}} \quad \Rightarrow \quad \frac{1}{2} \text{ M}$$

$$\therefore (10^6) = \frac{1}{2\pi\sqrt{200 \times 10^{-6} \times C}}$$

Squaring to both sides.

$$(10^6)^2 = \frac{1}{4\pi^2 \times 200 \times 10^{-6} \times C}$$

$$\therefore C = \frac{1}{(10^6)^2 \times 4\pi^2 \times 200 \times 10^{-6}}$$

$$\text{OR } \boxed{C = \frac{1.2665 \times 10^{-10} \text{ F}}{126.65 \text{ PF}}} \quad \Rightarrow \quad \frac{1}{2} \text{ M}$$

OR

* If value of 'R' is considered very high in comparison with inductor 'L' then

$$\therefore f_r = \frac{1}{2\pi\sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}} \quad \Rightarrow \quad \frac{1}{2} \text{ M}$$

Squaring to both sides

$$\therefore f_r^2 = \frac{1}{4\pi^2 \left[\frac{1}{LC} - \frac{R^2}{L^2} \right]}$$

$$\therefore f_r^2 * 4\pi^2 = \frac{1}{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$f_r^2 * 4\pi^2 + \frac{R^2}{L^2} = \frac{1}{LC}$$

$$(10^6)^2 * 4\pi^2 + \frac{(20)^2}{(200 \times 10^{-6})^2} = \frac{1}{LC}$$

SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

$$3.948 \times 10^{15} = \frac{1}{LC}$$

$$3.948 \times 10^{15} \times 200 \times 10^{-6} = \frac{1}{C}$$

$$C = 126.65 \text{ PF} \Rightarrow \text{1/2 M}$$

ii) The Q of the coil

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$= \frac{1}{20} \sqrt{\frac{200 \times 10^{-6}}{126.65 \times 10^{-12}}}$$

$$Q = 62.832 \Rightarrow \text{1 M}$$

OR

$$Q = \frac{X_L}{R} = \frac{2\pi f L}{R} = \frac{2\pi \times 10^6 \times 200 \times 10^{-6}}{20}$$

$$Q = 62.832 \Rightarrow \text{1 M}$$

iii) The current in each branch of the circuit at resonance
 Since this is a parallel circuit. We presume the applied voltage will be across each reactive element.

$$i) X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 10^6 \times 126.65 \times 10^{-12}} = 1.256 \text{ k}\Omega$$

$$ii) X_L = 2\pi f L = 2\pi \times 10^6 \times 200 \times 10^{-6} = 1.256 \text{ k}\Omega \Rightarrow \text{1 M}$$

$$I_C = \frac{V}{X_C} = \frac{20}{1.256 \times 10^3} = 15.92 \text{ mA} \Rightarrow \text{1 M}$$

$$I_L = \frac{V}{X_L} = \frac{20}{1.256 \times 10^3} = 15.92 \text{ mA} \Rightarrow \text{1 M}$$

b) Find current through impedance $3 + j5$ using superposition theorem in the circuit as shown in Fig. No. 7.

6M



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code **22330**

27

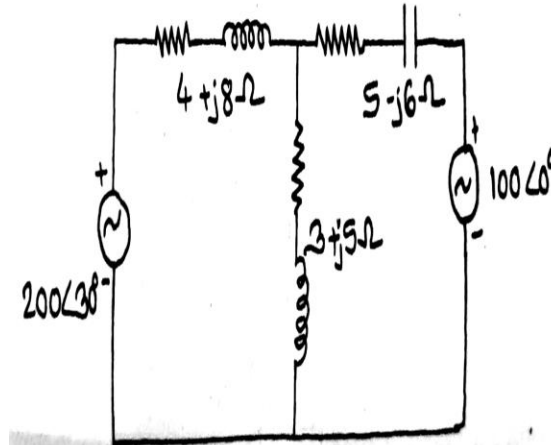


Fig. No. 7

SUMMER-19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

Ans:

Q.5 b)

Step 1: - convert V_1 & V_2 into rectangular form

$$V_1 = 200 \angle 30^\circ = 173.21 + j100$$

$$V_2 = 100 \angle 0^\circ = 100 + j0$$

find the current thr^{ough} Branch 'AB' as I_1 due to source $V_1 = 200 \angle 30^\circ$

\Rightarrow 2 Marks

The impedances $(5-j6)\Omega$ and $(3+j5)\Omega$ are in parallel and this combination is in series with $(4+j8)\Omega$

$$R_{Th} = \frac{(5-j6) * (3+j5)}{(5-j6) + (3+j5)} = \frac{15 + j25 - j8 + 30}{8-j1}$$

$$= \frac{45 + j7}{8-j1} = \frac{45.54 \angle 8.84^\circ}{8.062 \angle -7.13^\circ}$$

$$R_{Th} = 5.65 \angle 15.97^\circ$$

$$I_1 = \frac{200 \angle 30^\circ}{5.65 \angle 15.97^\circ}$$

$$\therefore I_1 = 35.398 \angle -14.03^\circ$$

$$I_1' = \frac{(5-j6)}{(5-j5) + (3+j5)} * I_1 = \frac{5-j6}{8-j1} * 35.398 \angle -14.03^\circ$$

$$= \frac{7.810 \angle -50.19^\circ}{8.062 \angle -7.13^\circ} * 35.398 \angle -14.03^\circ$$

$$I_1' = 34.28 \angle -57.09^\circ$$

Scanned by CamScanner




SUMMER-19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

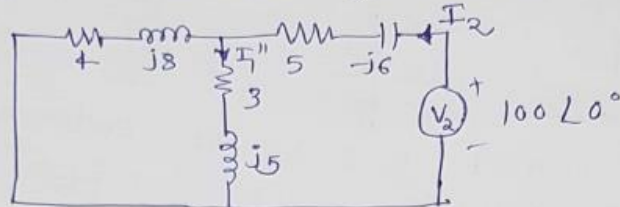Step 2 :- Similarly find current thr AB Branch
Due to source $V_2 = 100 \angle 0^\circ$



The impedances $(4+j8)\Omega$ & $(3+j5)\Omega$ are in parallel & this combination is in series with $(5-j6)\Omega$

$$R_{th} = \frac{(4+j8)(3+j5)}{(4+j8)(3+j5)} = \frac{12+j20+j24-40}{(7+j13)}$$

$$= \frac{-28+j44}{7+j13} = \frac{52.15 \angle 122.47^\circ}{14.765 \angle 61.69^\circ}$$

$$\therefore R_{th} = 3.532 \angle 60.78^\circ$$

$$I_2 = \frac{100 \angle 0^\circ}{3.532 \angle 60.78^\circ}$$

⇒ 2 Marks

$$I_2 = 28.32 \angle -60.78^\circ$$

$$I_1'' = \frac{(4+j8)}{(7+j13)} * I_2$$

$$= \frac{(4+j8)}{(7+j13)} * 28.32 \angle -60.78^\circ$$

$$= \frac{8.944 \angle 63.43^\circ}{14.765 \angle 61.69^\circ} * 28.32 \angle -60.78^\circ$$

$$= \frac{8.944 * 28.32 \angle 63.43^\circ + (-60.78^\circ)}{14.765 \angle 61.69^\circ}$$

$$I_1'' = \frac{253.29 \angle 2.65^\circ}{14.765 \angle 61.69^\circ}$$

$$I_1'' = 17.15 \angle -59.04^\circ$$

SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

Step 3:- current flowing thr^h AB branch due to

V_1 is $I_1' = 34.28 \angle -57.09$

V_2 is $I_1'' = 17.15 \angle -59.04$

convert these currents into Rectangular form

$I_1' = 18.63 - j28.78$

$I_1'' = 8.823 - j14.71$

$\therefore I_{AB \text{ Branch}} = I_1' + I_1''$

$\therefore I_{AB \text{ Branch}} = I_1' + I_1''$ or c/n thr^h $(3+j5)$ Branch

$= 27.453 - j43.49$

$\therefore I_{AB \text{ Branch}} \stackrel{m}{=} I_{(3+j5)} = 51.48 \angle 57.74$

2 Marks

c) Sketch the phasor diagram for the nominal drawn circuit with justification of each phasor drawn.

6M

Ans: Consider series R-L circuit

Phasor diagram of RL circuit

Where V_R = Voltage across the resistor 'R'

V_L = Voltage across the inductor 'L'

V = Total Voltage of the circuit

Circuit diagram : 1 Mark

Phasor diagram : 3 Marks



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code: 22330

31

Explanation :-

In RL circuit Resistor 'R' & Inductor 'L' are connected in series with a voltage supply of V_s . Since both R & L are connected in series, so the current in both the elements of the circuit remains same.

$$\text{i.e. } I_R = I_L = I$$

Let V_R & V_L be voltage drop across resistor & inductor.

In Resistor, the voltage V_R & I_R are in phase. Whereas in inductor, the voltage V_L & current are not in phase. The voltage leads the current by 90° .

Explanation
:2Marks


Note: If the student has attempted to solve the question considering any one of the following circuits : Series R-C or R-L-C circuit or Parallel R-L or R-C or R-L-C circuit, give appropriate marks.

SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

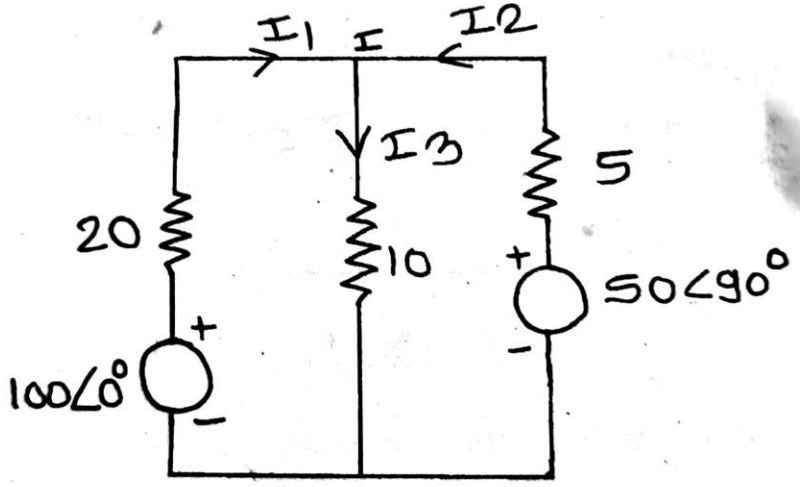Q. No.	Sub Q. N.	Answers	Marking Scheme
6.		Attempt any TWO of the following :	12- Total Marks
	a)	<p>Use nodal analysis to calculate the current flowing in each branch of the network shown in Fig. No. 8</p>  <p style="text-align: center;"><u>Fig. No. 8</u></p>	6M

SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

33

Ans:

Q.6 a) Using Nodal Analysis:

$100 \angle 0^\circ$
 $\Rightarrow 100 + j0$

$50 \angle 90^\circ \Rightarrow (0 + j50)$

Applying Nodal analysis to node 'A'

$$\frac{100 - V_A}{20} - \frac{V_A}{10} + \frac{j50 - V_A}{5} = 0 \Rightarrow \underline{\underline{1M}}$$

$$\frac{100 - V_A - 2V_A + j200 - 4V_A}{20} = 0$$

$$100 - 7V_A + j200 = 0$$

$$100 + j200 = 7V_A$$

SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

$\frac{100 + j200}{7} = V_A$

$\therefore V_A = 31.94 \angle 63.43^\circ \text{ V} \implies \text{1M}$

$\therefore V_A = 14.29 + j28.566$

(a) current flowing thr 20Ω resistor

$I_{20\Omega} = \frac{(100 \angle 0^\circ) - (31.94 \angle 63.43^\circ)}{20}$

$= \frac{100 + j0 - 14.29 - j28.57}{20}$

$= \frac{100 - 14.29 - j28.57}{20} = \frac{85.72 - j28.56}{20}$

$= \frac{90.35 \angle -18.42^\circ}{20} \implies \text{2M}$

$I_{20\Omega} = 4.517 \angle -18.42^\circ \text{ Amp.}$
or $4.285 - j1.427 \text{ Amp.}$

(b) current flowing thr 10Ω resistor

$I_{10\Omega} = \frac{V_A}{10} = \frac{31.94 \angle 63.43^\circ}{10}$

$\therefore I_{10\Omega} = 3.194 \angle 63.43^\circ \text{ Amp.} \implies \text{1M}$

(c) current flowing thr 5Ω resistor

$I_{5\Omega} = \frac{j50 - 14.29 - j28.57}{5}$

$= \frac{-14.29 + j21.43}{5}$

$= \frac{25.757 \angle 123.69^\circ}{5}$

$I_{5\Omega} = 5.151 \angle 123.69^\circ \text{ Amp.} \implies \text{1M}$

b) Verify the reciprocity theorem in the circuit given in Fig. No. 9

6M



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code: 22330

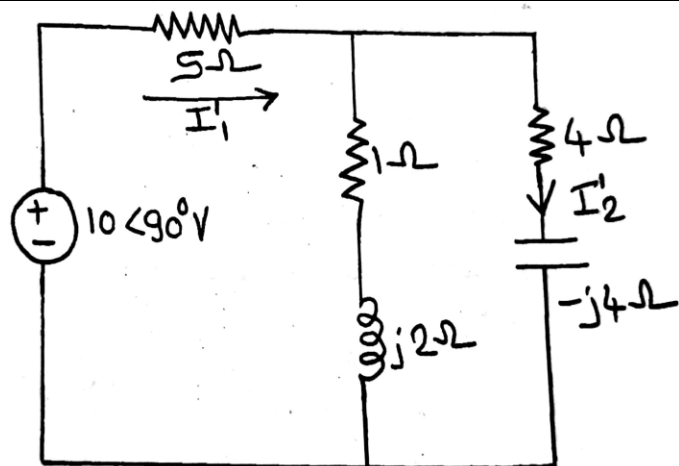


Fig. No. 9

Ans:


SUMMER-19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

Q6 b)

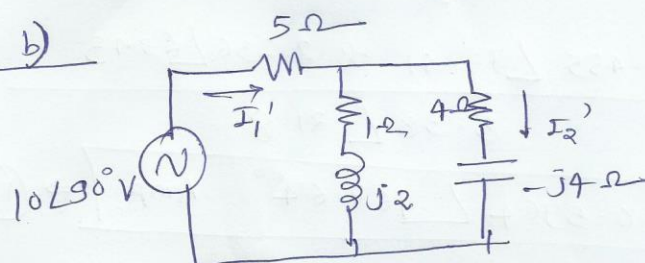

Case: 1
Step 1: consider the given circuit as it is

$$\begin{aligned} Z_{eq} &= 5 + [(1 + j2)] \parallel [(4 - j4)] \\ &= 5 + \frac{(1 + j2)(4 - j4)}{1 + j2 + 4 - j4} \\ &= 5 + \frac{(4 - j4 + j8 + 8)}{5 - j2} \\ &= 5 + \frac{12 + j4}{5 - j2} \\ &= \frac{25 - j10 + 12 + j4}{(5 - j2)} \\ &= \frac{37 - j6}{5 - j2} = \frac{37.48 \angle -9.21}{5.38 \angle -21.8} \end{aligned}$$

$$Z_{eq} = 6.966 \angle 12.59 \Omega \rightarrow (1M)$$

$$I_1' = \frac{10 \angle 90^\circ}{6.966 \angle 12.59} = 1.435 \angle +77.41 \text{ Amp.} \rightarrow (1M)$$

using c/n division rule,

$$\begin{aligned} I_2' &= 1.435 \angle 77.41 * \frac{(1 + j2)}{1 + j2 + 4 - j4} \\ &= \frac{1.435 \angle 77.41 * (1 + j2)}{5 - j2} \end{aligned}$$

SUMMER-19 EXAMINATION

Subject Name: Electric circuits and network


Model Answer

Subject Code 22330

$$= \frac{1.435 \angle 77.41^\circ \times 2.236 \angle 63.43^\circ}{5.38 \angle -21.8^\circ}$$

$$I_2' = 0.5964 \angle 162.64^\circ \text{ Amp} \Rightarrow (1M)$$

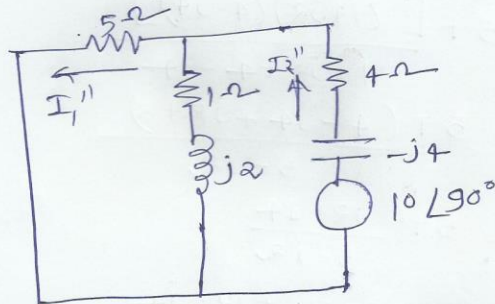Case 2: Change the position of voltage source
Step 1:- calculate currents.



$$Z_{eq}' = \frac{5 + j10}{6 + j2} + (4 - j4)$$

$$= \frac{11.18 \angle 63.43^\circ}{6.32 \angle 18.43^\circ} + (4 - j4)$$

$$= (1.718 \angle 45^\circ) + (4 - j4)$$

$$= 1.25 + j1.25 + 4 - j4$$

$$= 5.25 - j2.75$$

$$Z_{eq}' = 5.926 \angle -27.64^\circ \Rightarrow (1M)$$

SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

38

$$I_2'' = \frac{10 \angle 90^\circ}{5.926 \angle -27.61}$$

$$I_2'' = 1.687 \angle 117.64 \text{ Amp}$$

using current division rule,

$$I_1'' = 1.687 \angle 117.64 * \frac{(1+j2)}{6+j2}$$

$$= \frac{1.687 \angle 117.64 * (2.236 \angle 63.43)}{6.32 \angle 18.43}$$

$$I_1'' = 0.596 \angle 162.64 \text{ Amp} \Rightarrow (1M)$$

Proof :- per Reciprocity th^m statement,
As case: 1 Ratio of voltage source to response is

$$\frac{V}{I_2'} = \frac{10 \angle 90^\circ}{0.596 \angle 162.64}$$

$$= 16.77 \angle -76.64 \Rightarrow (1M)$$

Case: 2 $\frac{V_1}{I_1''} = \frac{10 \angle 90^\circ}{0.596 \angle 162.64}$

$$= 16.77 \angle -76.64$$

As the transfer ratio is same in both cases.
Thus the Reciprocity th^m is verified.



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code **22330**

39

	c)	<p>Draw the two port network and determine the indicated parameters for the following configurations:</p> <ul style="list-style-type: none">(i) Cascade configurations (ABCD parameter)(ii) Series configurations(iii) Parallel configurations.	6M

SUMMER- 19 EXAMINATION


Subject Name: Electric circuits and network

Model Answer


Subject Code 22330

Ans:

Cascade configuration ABCD parameter :-

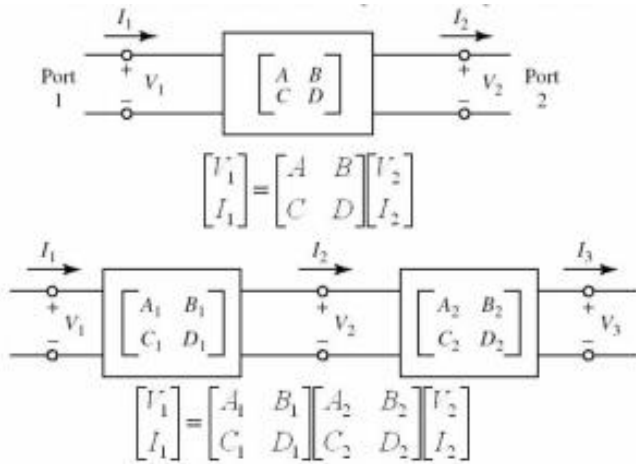


OR

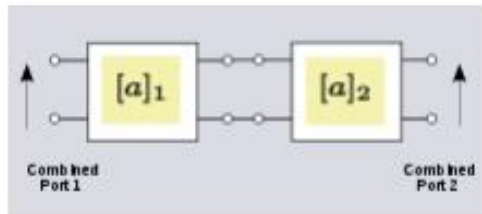


1 mark for the diagram and 1 mark for equation for each configuration

Series configurations:-

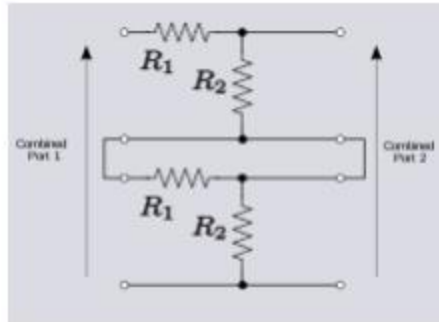

OR

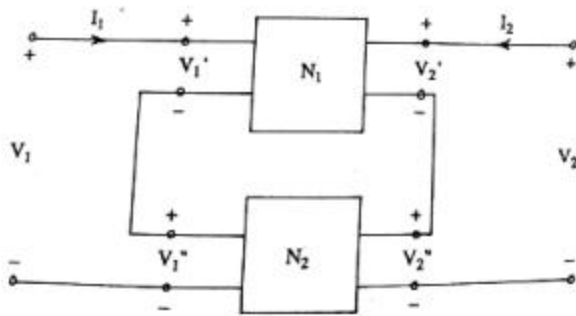

Where N1 and N2 are two port Network


$$[Z] = [Z_1] + [Z_2]$$

The Z parameter equation can be written as below

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

where Z_{11} , Z_{12} , Z_{21} and Z_{22} are sum of corresponding values of individual networks.

Parallel configurations:-

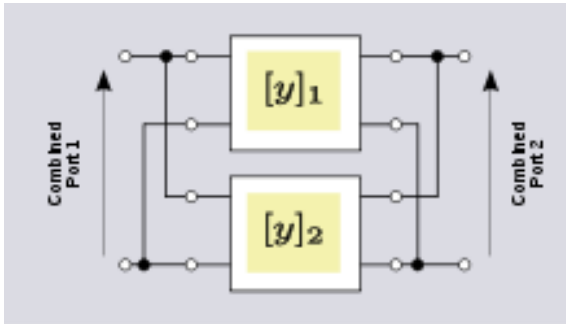

When two-ports are connected in a parallel configuration as shown in figure, The choice of two-port parameter is the y-parameters. The y-parameters of the combined network are found by matrix addition of the two individual y-parameter matrices.

$$[\mathbf{y}] = [\mathbf{y}]_1 + [\mathbf{y}]_2$$

Where Y parameter equation can be written as below

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

where Y_{11} , Y_{12} , Y_{21} and Y_{22} are sum of corresponding values of individual networks.