

22330

21222

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

15 minutes extra for each hour

- Instructions* – (1) All Questions are *Compulsory*.
- (2) Answer each next main Question on a new page.
- (3) Illustrate your answers with neat sketches wherever necessary.
- (4) Figures to the right indicate full marks.
- (5) Assume suitable data, if necessary.
- (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
- (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

- 1. Attempt any FIVE of the following: **10****
- a) Define -
- i) Apparent power
- ii) Reactive power
- b) Draw the phasor diagram for series RL and series RC circuit.
- c) Write the formula of resonance frequency and Q factor of parallel RLC circuit.
- d) State the formulae for star to delta conversion.
- e) Define the following term.
- i) Mesh
- ii) Node
- f) State the reciprocity theorem
- g) Write the ABCD parameter of two port network.
- P.T.O.

2. Attempt any THREE of the following: 12

- a) A series RL circuit takes a current of 2.7A. when connected to 240V, 50Hz a.c supply and consumes 350 watt. Calculate resistance inductance, impedance and power factor.
- b) An RLC series circuit with resistance of 20Ω , inductance 0.25H and capacitance of $100\mu\text{F}$ is supplied with 240V A.C. supply Calculate
 - i) resonance frequency
 - ii) current at this condition
 - iii) power factor
 - iv) quality factor
- c) Three resistance each of 12Ω are connected in star convert it into equivalent delta connection.
- d) Find value of 'I' of Fig. No. 1 using superposition theorem.

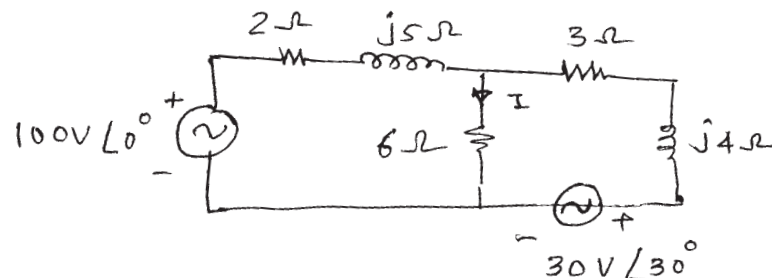


Fig. No. 1

3. Attempt any THREE of the following: 12

- a) A resistance of 10Ω , inductance of 0.1H and capacitance of $100\mu\text{f}$ are connected in series across 100V, 50Hz a.c. supply Calculate
 - i) current
 - ii) power factor
 - iii) power and draw vector diagram
- b) Compare series and parallel resonance circuit (any four points).

- c) Give the stepwise procedure for finding current using mesh analysis.
- d) Derive the condition so that power transferred from source to load is maximum.

4. Attempt any THREE of the following: 12

- a) Two impedances $Z_1 = 6 + j8\Omega$ and $Z_2 = 3 - j4\Omega$ are connected in parallel across 220V, 50 Hz, 1 ϕ AC. Calculate admittance of each branch, total admittance and supply current.
- b) Explain the concept of initial and final condition. State the meaning of $t = 0^-$ and $t = 0^+$
- c) Derive the expression for resonance frequency of series RLC circuit.
- d) Determine the current through 20Ω resistance in Fig. No. 2 using node analysis.

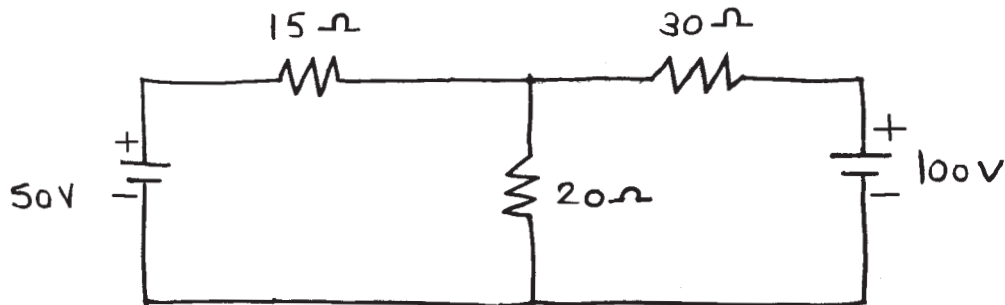


Fig. No. 2

- e) Calculate the value of current in 5Ω resistance using Norton's theorem for network shown in Fig. No. 3.

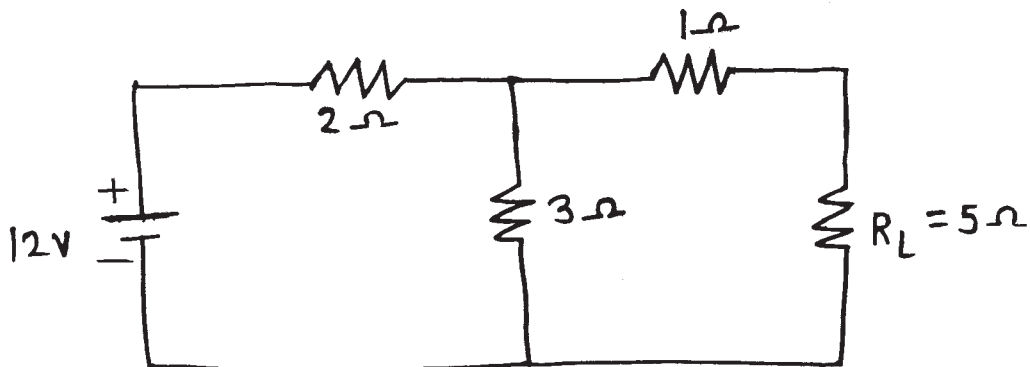
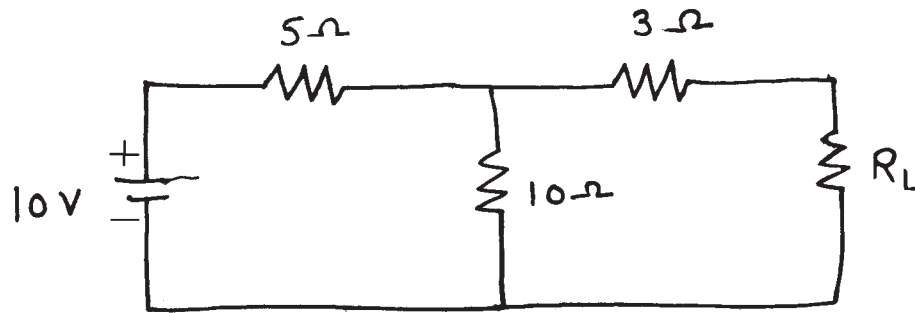


Fig. No. 3

5. Attempt any TWO of the following:

12

- a) A parallel circuit consist of a coil of $R = 10\Omega$ and $L = 0.2H$ is connected in parallel with capacitor of $50\mu F$. The circuit is supplied with $200V$, $50Hz$. Calculate the frequency at which the circuit behaves as a pure resistance and also find Q factor.
- b) Find the value of load resistance R_L to get maximum power transfer to it a shown in Fig. No. 4. Also find P_{max} .


Fig. No. 4

- c) Explain 'Z' parameter of two port network.

6. Attempt any TWO of the following:

12

- a) i) Explain with suitable example converting practical current source into equivalent voltage source.
ii) Practical voltage source into equivalent current source.
- b) State and explain Thevenin's theorem with suitable example.
- c) Find the short circuit admittance (Y) parameters for the network shown in Fig. No. 5.

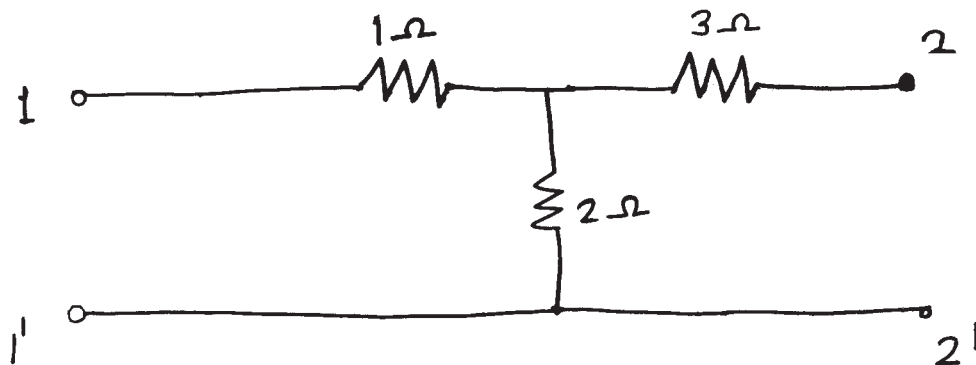Fig. No. 5