

22330

11819

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
  - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

1. Attempt any FIVE of the following :

10

- (a) Define :
  - (i) Admittance
  - (ii) Conductance
- (b) Write the equation of open circuit Z parameter.
- (c) Draw phasor diagram for R-L series circuit.
- (d) Draw resonance curve for series resonance.
- (e) Define :
  - (i) Node
  - (ii) Branch
- (f) State Thevenins theorem.
- (g) Write the formula for Delta to Star conversion giving examples.

[1 of 4]

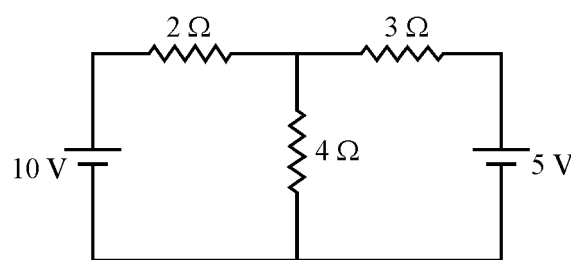
P.T.O.

**2. Attempt any THREE of the following :****12**

- (a) For RLC series circuit draw voltage triangle, power triangle and impedance triangle along with proper labellings and equations for condition  $V_L > V_C$ .
- (b) Define and state equations for (i) Active Power (ii) Reactive Power (iii) Apparent Power
- (c) Explain the steps for converting practical voltage source into practical current source.
- (d) Three resistances  $32 \Omega$ ,  $40 \Omega$ ,  $48 \Omega$  are connected in star circuit. Determine its equivalent delta circuit.

**3. Attempt any THREE of the following :****12**

- (a) If  $Z_1 = 3 + j7$  and  $Z_2 = 12 - j16$  are connected in parallel. Find the equivalent impedance of combination.
- (b) Determine Bandwidth and Quality factor (Q) for the series circuit.
- (c) Using Mesh Analysis find current through  $4 \Omega$  resistance. (Refer fig. 1)

**Fig. 1**

- (d) Explain the procedure for solving Thevenins theorem using suitable example.

4. Attempt any THREE of the following :

12

- (a) A coil has resistance of  $4 \Omega$  and an inductance of  $9.55 \text{ mH}$ . Calculate  
 (i) Reactance (ii) The impedance (iii) The current taken from  $240 \text{ V}$ ,  $50 \text{ Hz}$  supply.
- (b) Draw the phasor diagrams for a series RL and series RC with AC supply.
- (c) Compare series and parallel circuits.
- (d) Using source transformation technique find the resultant current ( $I$ ) through circuit. (Refer fig. 2)

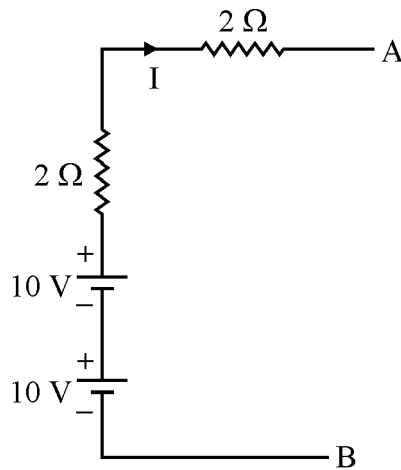


Fig. 2

- (e) Using super-position theorem find current through  $4 \Omega$  resistance. (Refer fig. 3)

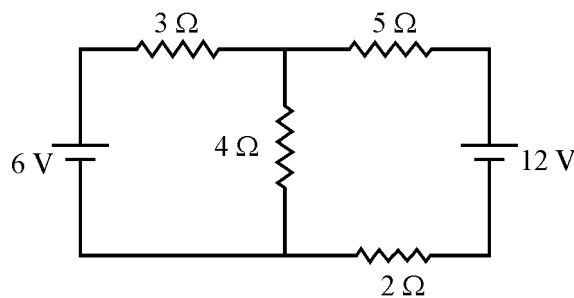


Fig. 3

P.T.O.

5. Attempt any TWO of the following :

12

- (a) Derive the expression for resonance frequency for parallel circuit.  
 (b) Calculate current through  $8\ \Omega$  resistance using Norton's theorem. (Refer fig. 4)

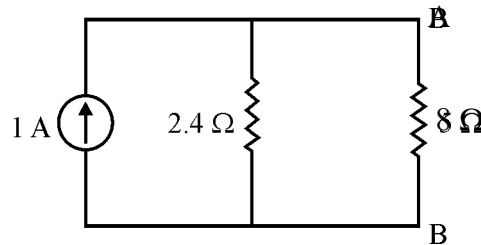


Fig. 4

- (c) Explain 'Π' and 'T' circuit with proper phasor diagram.

6. Attempt any TWO of the following :

12

- (a) Calculate the nodal voltage  $V_B$  using nodal analysis. (Refer fig. 5)

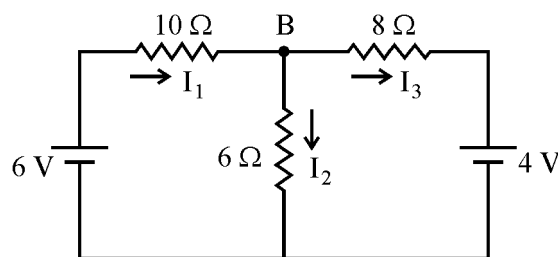


Fig. 5

- (b) State and explain :  
 (i) Maximum power transfer  
 (ii) Reciprocity theorem
- (c) Explain significance of two-port network. Also draw two port network for  
 (i) Cascade configuration ABCD parameter (ii) Series configuration.
-