

22421

11920

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
  - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

**1. Attempt any FIVE of the following :**

**10**

- (a) Sketch symbol and write truth table of two input EX-OR gate.
- (b) Define the term 'Multiplexer'. State two examples of multiplexer.
- (c) Implement T flip flop using J K flip flop. Write its truth table.
- (d) Implement following Boolean equation using fundamental gates :  
$$Y = ABC + A\bar{B}C + \bar{A}\bar{C}B$$
- (e) Identify direct addressing instructions from following instructions :
  - (i) MOV R0, R5
  - (ii) MOV R0, 80 H
  - (iii) MOV R0, #75H
  - (iv) ADD A, 45 H

[1 of 4]

P.T.O.

- (f) If initial content of accumulator is 44 H, find out the new content of accumulator after execution of the instruction

RR A

- (g) Find out number of data lines required to interface 16 LEDs arrange in the  $4 \times 4$  matrix form.

**2. Attempt any THREE of the following :**

**12**

- (a) Define following terms related to logic families :
- (i) Noise Margin
  - (ii) FAN-OUT
  - (iii) Propagation delay
  - (iv) Power dissipation
- (b) State Demorgan's theorem's and prove both theorems using truth table.
- (c) State functions of preset, clear, clock and SR inputs related to SR flip flop.
- (d) Sketch diagram of 4 bit asynchronous counter using suitable flip flop. Sketch timing diagram.

**3. Attempt any THREE of the following :**

**12**

- (a) List out any four assembler directives and state their functions.
- (b) Sketch diagram showing interfacing of two chips of RAM having size  $2k \times 8$  to 8051 microcontroller. Write its memory map.
- (c) Minimize following Boolean equation using 'k' map :
- $$Y = A \bar{B} C + \bar{A} \bar{B} C + \bar{A} \bar{B} \bar{C} + ABC$$
- and implement using basic gates.
- (d) List out three types of buses. State their functions.

- 4. Attempt any THREE of the following :** **12**
- (a) List out features of any four addressing modes of 8051.
  - (b) With the help of PCON register, explain Power down mode and Idle mode of 8051.
  - (c) Construct full adder circuit using K map.
  - (d) Justify 'NOR gate is called as universal gate'. Sketch relevant diagram.
  - (e) Compare microprocessor with microcontroller on the basis of any four factors.
- 5. Attempt any TWO of the following :** **12**
- (a) Explain with neat diagram microcontroller based water level controller.
  - (b) Develop ALP for 8051 to perform addition, anding, multiplication of two data – Data-1 is at memory location 55 H and Data 2 is 20 H. Store result at internal memory locations.
  - (c) Explain internal and external memory organisation of 8051.
- 6. Attempt any TWO of the following :** **12**
- (a) Explain functions of all pins of Port 0, Port 1, Port 2 and Port 3.
  - (b) Sketch diagram showing interfacing of single 7-segment common Anode display to 8051. Develop ALP to display number '7,' on it.
  - (c) Convert following Boolean equation to standard SOP form and implement using NAND-NAND logic.
    - (i)  $y = A \bar{B} C + ABC \bar{D} + A \bar{C} D$
    - (ii)  $y = PQ + PQR + PQ \bar{R}$
-

