



22421

12223

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks****1. Attempt any FIVE of the following :****10**

- (a) Draw the switching circuit analogy of an AND gate, symbol, Truth Table and logic expression.
- (b) In the K-map, list all the grouping methods with its eliminating variable count.
- (c) How to convert SR flip-flop into D flip-flop ? Draw circuit diagram and truth table of D flip-flop.
- (d) Explain : (i) Fan-in (ii) Fan-out with respect to logic families.
- (e) Identify the addressing mode of the instruction :
  - (i) MOV X @ Ro, A
  - (ii) CJNE A, # data, rel



- (f) Explain working of XCHD instruction with syntax and example.
- (g) Find the number of address lines required for :
  - (i) 4 K RAM
  - (ii) 8 K ROM

**2. Attempt any THREE of the following :**

**4 × 3 = 12**

- (a) Prove NOR gate as universal gate with suitable diagrams.
- (b) Design full Adder using K-map. Draw circuit diagram & with Truth Table.
- (c) Minimize the following Boolean expression using K-map and realize it using the basic gates.  $\gamma_{(A,B,C,D)} = \Sigma m (1,3,5,9,11,13)$
- (d) Convert following equation into canonical required POS OR SOP form :
  - (i)  $\gamma = (\bar{A} + B)(B + \bar{C})(\bar{A} + \bar{C})$
  - (ii)  $\gamma = A + BC + ABC$

**3. Attempt any THREE of the following :**

**4 × 3 = 12**

- (a) Describe any four addressing modes of 8051 microcontroller with suitable example.
- (b) Draw and explain the interfacing of 16 × 2 LCD display with 8051.
- (c) Implement the following logic function using suitable multiplexer :  
 $F(A,B,C) = \Pi M (0, 1, 2, 5, 7)$
- (d) Draw the architecture of 8051 and label various blocks.

**4. Attempt any THREE of the following :**

**4 × 3 = 12**

- (a) Explain different program development steps in assembly language programming.
- (b) Compare 8051, 8031 and 8751 on the basis of different parameters.

- (c) Realize the following expression using K-map and implement it :

$$Y_{(A,B,C,D)} = \Sigma m(0, 2, 3, 5, 6, 7, 10, 11) + d(8, 14, 15)$$

- (d) Apply Boolean rules to simplify the following function :

$$G = (A + B) (A + \bar{B})$$

$$G = \bar{A} \bar{B} C + A \bar{B} C + A B \bar{C}$$

- (e) Draw and explain the flag register of 8051 microcontroller.

**5. Attempt any TWO of the following :**

**6 × 2 = 12**

- (a) Draw and explain the interfacing of 4 × 4 matrix keyboard with 8051 using ports.
- (b) Write a program to find how many ODD numbers are present in the array of 10 numbers stored in internal memory RAM with algorithm and flowchart.
- (c) Explain the various power saving options of 8051.

**6. Attempt any TWO of the following :**

**6 × 2 = 12**

- (a) What is the use of stack in 8051 micro controller and draw and explain the function of SCON register with each bit.
- (b) Develop an ALP for interfacing of LED's with port 1 of 8051. Draw interfacing for the same.
- (c) Explain triggering methods in Flip-Flops in brief and explain race around condition in JK Flip-Flop and how it is eliminated.
-

