

22421

23124

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.

Marks

1. Attempt any FIVE of the following :

5 × 2 = 10

- (a) Construct OR gate using NAND gate.
- (b) Define the term 'multiplexer'. State two examples of multiplexer.
- (c) Implement T flip-flop using JK flip-flop. Write its truth table.
- (d) Explain :
 - (i) Fan-in
 - (ii) Fan-outwith respect to logic families.
- (e) Define :
 - (i) Address bus
 - (ii) Data bus
- (f) Identify the addressing mode of the instruction :
 - (i) MOVX@Ro, A
 - (ii) CJNE A, # data, rel



- (g) Find the number of address lines required for
- (i) 4 K RAM
 - (ii) 8 K ROM

2. Attempt any THREE of the following :

3 × 4 = 12

- (a) State and explain De-Morgan's first theorem.
- (b) Design full adder using K-map. Draw circuit diagram with truth table.
- (c) Solve the following SOP expressions with the help of K-map :
 - (i) $F(A, B, C, D) = \Sigma m(0, 1, 3, 4, 5, 7)$
 - (ii) $F(A, B, C) = \Sigma m(0, 1, 4, 5, 6, 7)$
- (d) Write any two laws of Boolean algebra. Justify with the help of truth table.

3. Attempt any THREE of the following :

3 × 4 = 12

- (a) Explain any four addressing modes of 8051 microcontroller with one example each.
- (b) Sketch diagram showing interfacing of two chips of RAM having size $2\text{ K} \times 8$ to 8051 microcontroller. Write its memory map.
- (c) Minimize following Boolean equation using 'K' map : $Y = A\bar{B}C + \bar{A}\bar{B}C + ABC$ and implement using basic gates.
- (d) List any eight features of microcontroller 8051.

4. Attempt any THREE of the following :

3 × 4 = 12

- (a) Explain different program development steps in assembly language programming.
- (b) Compare between Harvard and Von-Neumann architecture. (any four points)
- (c) Design 3-bit binary to gray code converter.
- (d) Justify 'NOR gate is called as universal gate'. Sketch relevant diagram.
- (e) Draw and explain the flag register of 8051 microcontroller.

5. Attempt any TWO of the following : **2 × 6 = 12**

- (a) Explain with neat diagram microcontroller based water level controller.
- (b) Develop an ALP to generate square wave of 1 kHz at port pin 1.4. Draw flowchart for it.
- (c) Draw architecture of 8051 microcontroller.

6. Attempt any TWO of the following : **2 × 6 = 12**

- (a) Explain power saving options :
 - (i) Idle mode
 - (ii) Power down mode
 - (b) Develop an ALP for interfacing of LEDs with port 1 of 8051. Draw interfacing for the same.
 - (c) Construct 3 bit asynchronous up-counter using flip-flop. Draw its timing diagram.
-

