

# 22421

**12526**

**3 Hours / 70 Marks**

Seat No. 

--	--	--	--	--	--	--	--

- 
- Instructions* – (1) All Questions are *Compulsory*.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data, if necessary.
- (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
- (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

- 1. Attempt any FIVE of the following : **10****
- a) Construct NOR gate using NAND gate.
- b) Draw the symbol and truth table of X-NOR gate.
- c) Define minterm and maxterm.
- d) Define demultiplexer and state any two examples.
- e) Identity the addressing mode of the following instructions.
- i) `MOVX@Ro, A`
- ii) `MOV A, #30H`
- f) State the function of assembler and compiler.
- g) Find the number of address line required for –
- i) 4K RAM
- ii) 8K ROM

P.T.O.

- 2. Attempt any THREE of the following :** **12**
- a) State and verify Demorgans first and second theorem with truth table.
  - b) Compare the TTL, CMOS, ECL logic family on the basis of –
    - i) Fan-out
    - ii) Power dissipation
    - iii) Figure of merit.
    - iv) Propagation delay
  - c) Design 16:1 multiplexer using 4:1 multiplexer.
  - d) Explain 4 bit asynchronous up counter using diagram and truth table.
- 3. Attempt any THREE of the following :** **12**
- a) Solve the following SOP expression using K-map.  
 $f(A, B, C, D) = \Sigma m(0, 1, 3, 5, 7, 9)$
  - b) Compare microprocessor and microcontroller.
  - c) State and explain assembler directives.
  - d) Draw the interfacing diagram of  $16 \times 2$  LCD display.
- 4. Attempt any THREE of the following :** **12**
- a) State universal gates and explain why these gates are called as universal gates.
  - b) Explain full adder with neat diagram and truth table.
  - c) State any 8 features of 8051 microcontroller.
  - d) Explain power saving modes of 8051 microcontroller.
  - e) Explain software development cycle.

- 5. Attempt any TWO of the following :** **12**
- a) Draw the detailed architecture of 8051. State the function of stack pointer.
  - b) Develop an ALP to rotate the stepper motor  $90^\circ$  in anticlockwise direction with the neat diagram.
  - c) Develop an ALF to exchange the ten numbers from internal memory location 20H and 40H with flowchart and algorithm.
- 6. Attempt any TWO of the following :** **12**
- a) Explain master slave JK Flip Flop with diagram and truth table.
  - b) Compare Harvard and Von Neumann architecture. (4 points)  
State the function of address and data bus.
  - c) Develop an ALP to generate square wave of 2KHz on P3.0.  
Also draw the flowchart.
-