

# 22423

**22223**

**3 Hours / 70 Marks**

Seat No. 

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
  - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

- 1. Attempt any FIVE of the following: **10****
- a) Define :
    - i) Slew rate
    - ii) CMRR
  - b) Draw circuit diagram of non-inverting adder with 3 inputs.
  - c) List any four specifications of IC LM-324.
  - d) Give classification of filters.
  - e) Draw pin diagram of IC LM-324.
  - f) State any two applications of PLL.
  - g) Define the following terms with respect to filter :
    - i) Q factor
    - ii) Roll off rate

P.T.O.

2. Attempt any THREE of the following:

12

- Describe the function of intermediate stage and level shifter stage of op-amp with its block diagram.
- Draw and describe following op-amp based operation using log and antilog amplifier  $V_0 = V_1 \times V_2$ .
- Draw and explain the working of FM demodulator using PLL.
- If  $V_{in1} = 5\text{m Vrms}$  and  $V_{in2} = 10\text{ mVrms}$ , obtain the output voltage for open loop differential amplifier. Assume op-amp is 741 and voltage swing =  $\pm 14\text{V}$ . Also sketch output waveform.

3. Attempt any THREE of the following:

12

- Draw the closed loop inverting amplifier using op-amp and derive the expression for its gain.
- Identify the given circuit and explain with input-output waveforms. Refer Fig. No. 1.

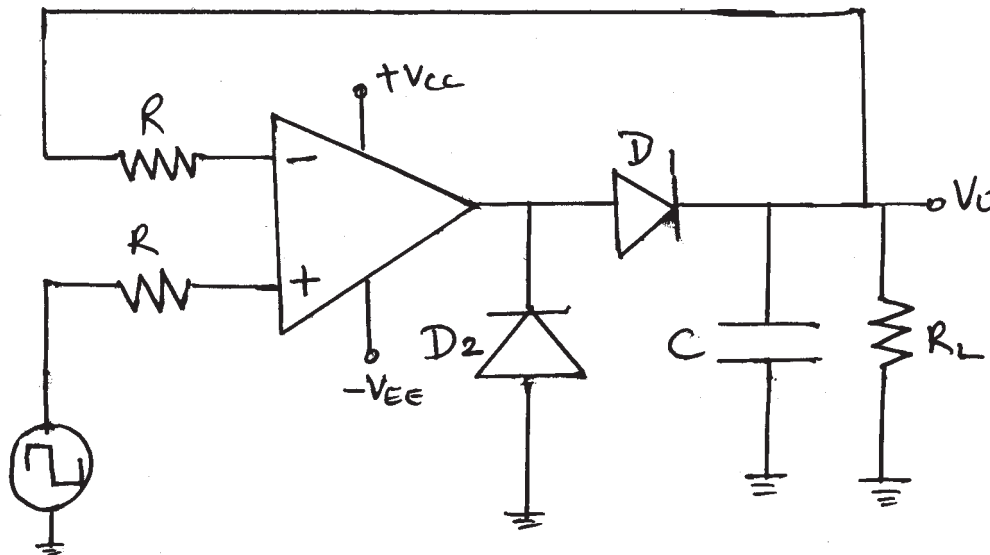


Figure No. 1.

- Design and draw 1st order high pass filter with cut off frequency 2 kHz and passband gain of 2.
- Draw circuit diagram of Bistable multivibrator using IC 555 and describe its working, working with waveforms.

**4. Attempt any THREE of the following: 12**

- a) Suggest op-amp based circuit to convert square wave to spikes and draw the circuit with input and output waveforms.
- b) Explain with circuit diagram, the procedure to null the offset voltage in op-amp.
- c) Design and draw the circuit for the following operation using op-amp.  $V_0 = -(V_1 + V_2 + V_3)$
- d) Derive the expression for output voltage of instrumentation amplifier using 3 op-amps.
- e) Determine pulse width of Monostable multivibrator using IC 555 timer for  $C = 0.047 \mu\text{F}$  and  $R = 56\text{k}\Omega$ .

**5. Attempt any TWO of the following: 12**

- a) Derive output equation for voltage to current converter with grounded load. Draw the circuit diagram.
- b) Draw second order high pass filter and describe its operation with frequency response characteristics. State the equations for cut off frequency and passband gain.
- c) For a schmitt trigger using op-amp, find threshold voltage  $V_{UTP}$  and  $V_{LTP}$  when  $R_2 = 150\text{k}\Omega$ ,  $R_1 = 100\text{k}\Omega$ .  $V_{in} = 500 \text{ mV}$ , sine wave saturation voltage =  $\pm 15\text{V}$ . Also find hysteresis voltage.

6. Attempt any TWO of the following:

12

- a) Draw and describe working of Colpitt's oscillator with neat circuit diagram. Also compare Colpitt's oscillator with Hartley oscillator with respect to
  - i) Frequency of oscillation formula
  - ii) Components used
- b) Explain the operation of sample and hold circuit with neat diagram. Draw the input-output wave forms.
- c) Identify and sketch op-amp based filter circuit to fulfill the following frequency response. Draw its ideal characteristics. Refer Fig. No. 2.

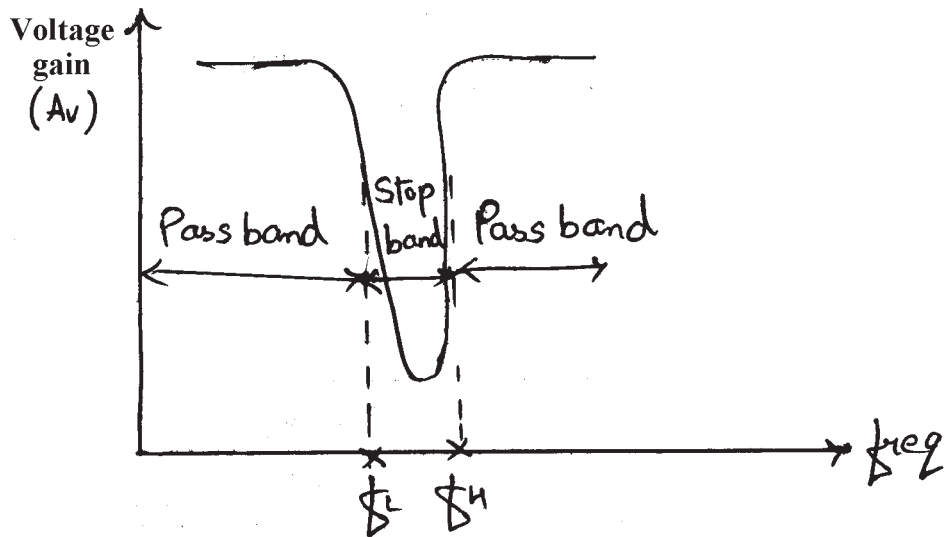


Figure No. 2.