

22423

12223

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

- 1. Attempt any FIVE of the following: **10****
- a) Define Input offset voltage and Input bias current.
 - b) Draw the circuit diagram of voltage follower.
 - c) Draw pin diagram of IC 565.
 - d) Define cutoff frequency and passband.
 - e) List two applications of IC LM324.
 - f) Draw circuit diagram of I to V converter.
 - g) State two merits of active filters over passive filters.

P.T.O.

2. Attempt any THREE of the following: 12

- Describe the operation of PLL as FM demodulator.
- Sketch first order Butterworth low pass filter with component value at cutoff frequency of 15 kHz with passband gain of 2.
- In op-amp based Schmitt trigger, $R_2 = 200\Omega$, $R_1 = 50\Omega$
 $V_{in} = 500 \text{ mV}_{PP}$ sine wave, saturation voltage = $\pm 5 \text{ V}$.
 Determine threshold Voltage V_{UTP} , V_{LTP} .
- Draw ideal and practical voltage transfer curve of op-amp.

3. Attempt any THREE of the following: 12

- Draw block diagram of OPAMP and state function of each block.
- Draw the circuit of basic differentiator and derive output expression.
- Draw a neat circuit diagram of analog divider using log-antilog amplifiers and explain its operation.
- Draw filter circuit for the following response. (Refer Fig. 1)

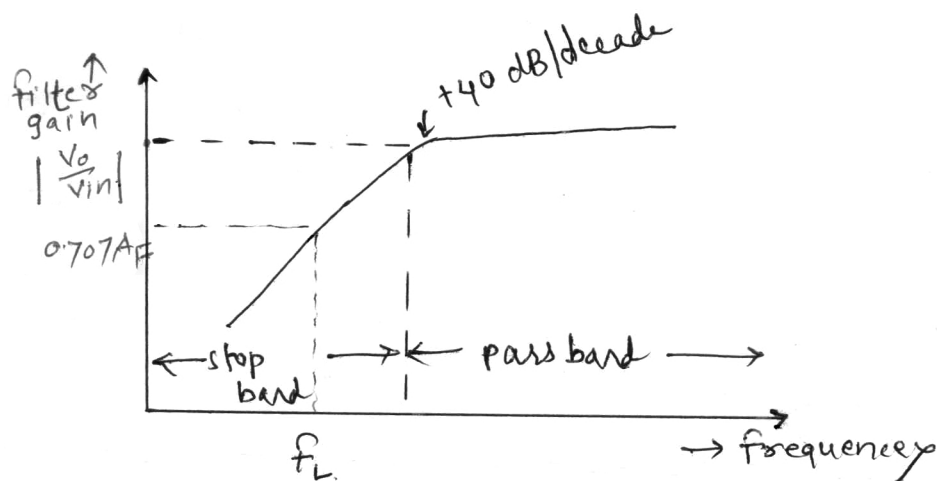


Fig. No. 1

- 4. Attempt any THREE of the following:** **12**
- a) Compare open loop and closed loop configuration.
 - b) Explain the procedure to null the offset voltage with appropriate diagrams.
 - c) Design the circuit to get the output voltage.
 $V_0 = 3V_1 + 2V_2$ where
 V_1 and V_2 are input voltages.
 - d) Explain phase shift oscillator using IC 741 with neat diagram.
 - e) Explain the working of astable multivibrator using IC 555.
- 5. Attempt any TWO of the following:** **12**
- a) Draw a circuit diagram of V-I converter of floating load. Derive expression for its output. List any two applications.
 - b) Sketch input and output waveform for 2V peak to peak size wave for Inverting ZCD and active Integrator.
 - c) Design second order high pass Butterworth filter with higher cutoff frequency of 1.5 kHz. Draw circuit with component values.
- 6. Attempt any TWO of the following:** **12**
- a) Calculate output voltage for open loop non-inverting amplifier. If $V_{in} = 10$ mv dc, also draw input and output waveform and draw circuit diagram also.
 - b) Explain operation of Instrumentation amplifier with two op-amp with neat diagram.

- c) From the circuit diagram given in Fig. 2, identify the name of the circuit and calculate cut off frequency and pass band gain.

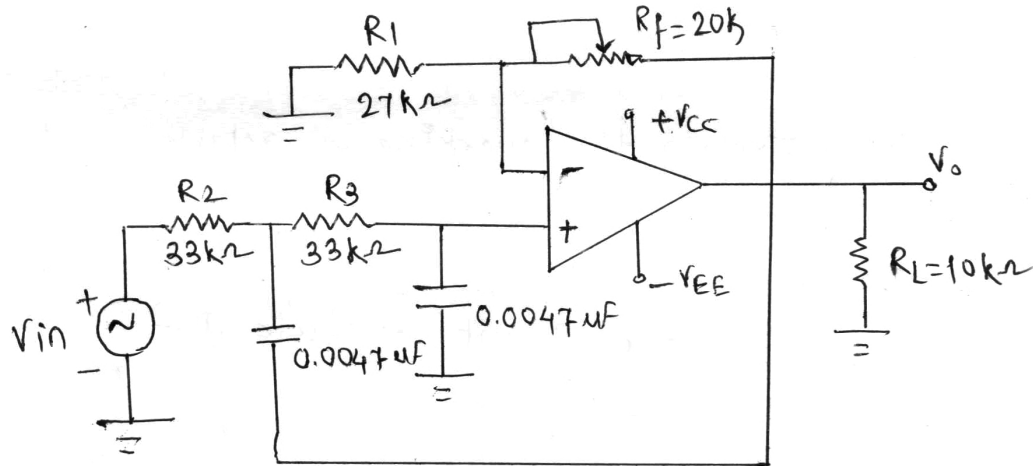


Fig. No. 2