

22427

21222

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

15 minutes extra for each hour

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.

Marks

1. **Attempt any FIVE :**

(5 × 2 = 10)

- (a) State two applications of power MOSFET.
- (b) Draw the symbol of PUT and GTO.
- (c) Define commutation and state its types.
- (d) Define inverter and state its types.
- (e) Draw the block diagram of UPS.
- (f) State two advantages of gate triggering.
- (g) Define firing angle and conduction angle.

2. **Attempt any THREE :**

(3 × 4 = 12)

- (a) Draw the constructional details of IGBT and mark the layers.
- (b) Describe the operation of a battery charger with neat diagram.
- (c) With a neat diagram explain the operation of step down chopper using MOSFET.
- (d) Draw and explain complementary commutation circuit.

3. Attempt any THREE : **(3 × 4 = 12)**

- (a) Draw the circuit diagram of 1 ϕ H.W.C. Rectifier with 'R' load. Explain the working with wave forms.
- (b) Draw and explain the operation of a triggering circuit to control the firing angle $0^\circ - 180^\circ$.
- (c) Draw and explain the operation of a light dimmer circuit using TRIAC & DIAC.
- (d) Suggest a suitable inverter to produce square wave output. Draw its neat circuit diagram.

4. Attempt any THREE : **(3 × 4 = 12)**

- (a) Draw and explain two transistor analogy of SCR.
- (b) A single phase full wave controlled rectifier is supplied with a voltage $V=100 \sin(314 t)$, $\alpha = 30^\circ$ and load resistance is 50Ω . Find the average output DC voltage and load current.
- (c) Describe the effect of free wheeling diode with respect to single phase center tapped fully controlled rectifier with RL load.
- (d) Draw and explain the operation of a temperature control circuit using SCR.
- (e) Draw the constructional detail of GTO. Explain its working principle.

5. Attempt any TWO : **(2 × 6 = 12)**

- (a) Draw the constructional details of TRIAC. State its mode of operation and explain its V-I characteristics.
- (b) Explain the operation of three phase half wave controlled rectifier with circuit diagram. Draw i/p – o/p wave forms.
- (c) Explain the operation of series inverter with neat circuit diagram. Draw the waveforms.

6. Attempt any TWO :**(2 × 6 = 12)**

- (a) (i) Define chopper. State its classification.
 - (ii) Compare step-down and step-up chopper [any four points].
 - (b) Describe the operation of synchronized UJT triggering circuit with circuit diagram.
 - (c) (i) Draw neat labelled diagram of V-I characteristics of SCR.
 - (ii) Explain the effect of gate current on turn on voltage of SCR.
-

