

22427

22232

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.

**Marks**

1. Attempt any FIVE of the following :

5 × 2 = 10

- (a) Draw labelled symbol of LASCR and SBS.
- (b) State two applications of TRIAC.
- (c) List two types of gate trigger circuits.
- (d) State the relation between firing angle and conduction angle with waveform.
- (e) List two applications of inverter.
- (f) Define converter and state its types.
- (g) Draw the block diagram of on line UPS.

2. Attempt any THREE of the following :

3 × 4 = 12

- (a) Draw neat labelled diagram of V-I characteristics of SCR. Define holding current and latching current.
- (b) Draw and explain the block diagram of SMPS.



- (c) Explain with a neat circuit diagram, the operation of series inverter.
- (d) Explain with circuit diagram and waveform the operation of single phase centre tapped full wave controlled rectifier with R load.

**3. Attempt any THREE of the following :**

**3 × 4 = 12**

- (a) Explain with circuit diagram the operation of a suitable over current protection circuit for high power transistor.
- (b) Describe the effect of freewheeling diode with respect to single phase half wave controlled rectifier with RL load.
- (c) Name a suitable chopper to decrease the output voltage and also explain its operation with neat circuit diagram.
- (d) Explain with circuit diagram the operation of emergency lighting system.

**4. Attempt any THREE of the following :**

**3 × 4 = 12**

- (a) Describe the working of class C commutation with neat circuit diagram and waveforms.
- (b) A single phase fully controlled rectifier is supplied with voltage  $V=300 \sin 314 t$ . If firing angle  $\alpha = 60^\circ$ , Find
  - (i) average output DC voltage
  - (ii) load current for load resistance  $500\Omega$ .
- (c) Draw circuit diagram of step up chopper. State its output voltage expression and draw its input output waveforms.
- (d) Explain with circuit diagram the operation of a suitable circuit to charge a battery.
- (e) List different Turn ON methods of SCR and explain any one in detail.

**5. Attempt any TWO of the following :****2 × 6 = 12**

- (a) Draw labelled constructional diagram for DIAC and describe its operating principle with V-I characteristics.
- (b) Describe the operation of PUT as relaxation oscillator.
- (c) Draw the circuit diagram of three phase half wave controlled rectifier. Explain the working of it with input output waveforms.

**6. Attempt any TWO of the following :****2 × 6 = 12**

- (a) Explain with a neat circuit diagram the operation of parallel inverter.
  - (b) Draw labelled constructional diagram of SCR. Explain its operating principle with two transistor analogy.
  - (c) (i) Suggest a suitable power device which combines benefits of a power MOSFET and a BJT. Also draw its V-I characteristics.  
(ii) Suggest a suitable power device which can be turned OFF by applying negative pulse to its gate terminal. Also draw its labelled constructional diagram.
-

