

22427

23124

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE :

2 × 5 = 10

- (a) State any two applications of Power MOSFET.
- (b) Draw the symbol of UJT and TRIAC.
- (c) Define commutation and state its types.
- (d) Sketch the circuit diagram of series inverter.
- (e) Draw the block diagram of SMPS.
- (f) State two advantages of Class-C commutation.
- (g) Define firing angle and conduction angle.

2. Attempt any THREE :

3 × 4 = 12

- (a) Draw and explain V-I characteristics of DIAC.
- (b) Describe the operation of a Emergency lighting system with neat diagram.
- (c) With a neat diagram, explain the operation of step-up chopper.
- (d) Draw and explain Class-C complementary commutation circuit.



- 3. Attempt any THREE :** **3 × 4 = 12**
- (a) Draw the circuit diagram of 1ϕ half wave Rectifier with 'R' Load. Explain the working with waveforms.
 - (b) Explain the PUT as a relaxation oscillator.
 - (c) Draw and explain the operation of a light dimmer circuit using TRIAC & DIAC.
 - (d) Name a suitable chopper to increase the output voltage and explain its operation with neat circuit diagram.
- 4. Attempt any THREE :** **3 × 4 = 12**
- (a) Draw and explain two transistor analogy of SCR.
 - (b) A single phase full wave controlled rectifier is supplied with a voltage $V = 100 \sin (314t)$, $\alpha = 30^\circ$ and load resistance is 50Ω . Find the average output, DC voltage and load current.
 - (c) Draw the circuit diagram of single phase centre tapped full wave Rectifier with 'R' load. Explain the working with waveforms.
 - (d) Draw and explain the block diagram of On-line UPS.
 - (e) Draw the constructional details of GTO. Explain its working principle.
- 5. Attempt any TWO :** **2 × 6 = 12**
- (a) Draw the constructional details of power transistor and explain its V-I characteristics and give its application.
 - (b) Explain the operation of three phase half wave controlled rectifier with circuit diagram. Draw I/p and o/p waveforms.
 - (c) Explain the operation of parallel inverter with neat sketch. Draw the waveforms.
- 6. Attempt any TWO :** **2 × 6 = 12**
- (a) (i) Define Chopper. State its classification.
(ii) Compare step-down and step-up Chopper (any four points).
 - (b) (i) Draw neat labelled diagram of V-I characteristics of SCR.
(ii) Explain the effect of gate current on turn on voltage of SCR.
 - (c) State the need of protection circuit of SCR. Describe the working of snubber circuit with neat diagram.
-