



22526

12223

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.

Marks

1. Attempt any FIVE of the following :

10

- (a) Draw the symbols of following components used in industrial control circuits :
 - (i) Push button (NO)
 - (ii) Selector Switch
 - (iii) Relay
 - (iv) Pressure Switch
- (b) Give the classification of PLC.
- (c) State the need of automation.
- (d) Define bit and word.
- (e) State any two uses of HMI.
- (f) Draw ladder diagram of seal-in-circuit w.r.t. PLC.
- (g) Draw the ladder diagram for verifying the NAND and NOR logic.



2. Attempt any **THREE** of the following :


12

- (a) Compare between Power and Control circuit. (Any 4 points)
- (b) Describe DC input module with neat block diagram.
- (c) Draw a ladder diagram for 2 lamps having following conditions :
 - (i) Start Push button turn ON red lamp after 15 seconds yellow lamp turns ON.
 - (ii) Stop Push button turns OFF yellow lamp immediately and after 15 seconds Red lamp turns OFF.
- (d) Develop the ladder diagram for DOL starter with OLR.

3. Attempt any **THREE** of the following :

12

- (a) Explain the instruction for UP counter with waveform.
- (b) Describe monolithic SCADA architecture.
- (c) Develop the ladder diagram for PLC based water level controller.
- (d) Draw the timing diagram for following ladder program :

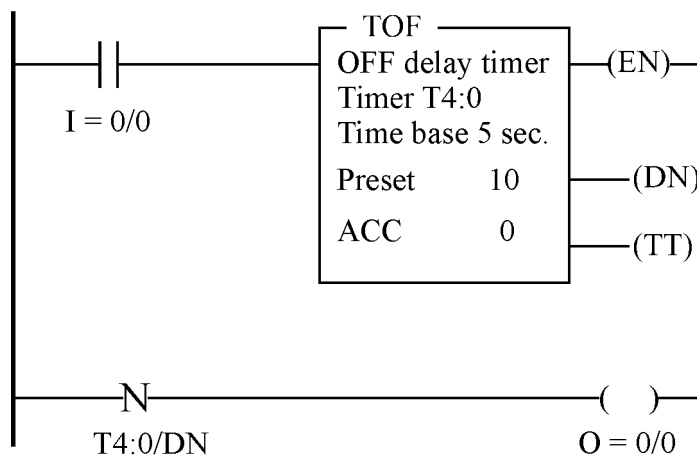

4. Attempt any **THREE** of the following :

12

- (a) Explain Latching Relay using PLC.
- (b) Explain speciality module of PLC –
 - (i) Communication module
 - (ii) PID controller module

- (c) Explain contactor with neat diagram.
- (d) Draw control and power circuit of Hoist control.
- (e) Describe analog input module with neat block diagram.

5. Attempt any TWO of the following :

12

- (a) Describe the block diagram of SCADA.
- (b) Explain the working of PLC based stepper motor control with the help of ladder diagram.
- (c) Develop a control and power circuit for automatic star-delta starter.

6. Attempt any TWO of the following :

12

- (a) Develop a ladder program for following conditions :
 - (i) Start push button starts motor M1, M2 and M3 immediately.
 - (ii) Stop push button stops motor M1 immediately and after 15 seconds motor M2 stops.
 - (iii) When motor M2 stops, after 15 seconds motor M3 stops.
 - (b) Explain the working of PLC based Traffic Light Control with the help of ladder program.
 - (c) Draw the block diagram of PLC and explain the function of each block.
-

