

## Scheme - I

### Sample Question Paper

**Program Name** : Electrical Engineering Program Group  
**Program Code** : EE/EP/EU  
**Semester** : Fifth  
**Course Title** : Power Electronic Applications (Elective)  
**Max. Marks** : 70

**22527**

**Time: 3 Hrs.**

---

#### Instructions:

- (1) All questions are compulsory.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Sub-questions in a main question carry equal marks.
- (5) Assume suitable data if necessary.
- (6) Preferably, write the answers in sequential order.

#### Q.1) Attempt any Five of the following.

**10 Marks**

- a) Draw labeled transfer characteristics of Power MOSFET.
- b) Define forward break over voltage of SCR.
- c) List any two applications of IGBT.
- d) Write the different types of inverter.
- e) List four switching components used in inverters.
- f) Write any two applications of dual converters.
- g) List the types of high frequency heating.

#### Q.2) Attempt any Three of the following.

**12 Marks**

- a) Explain with a neat labeled sketch the working principle of the single phase parallel inverter.
- b) Explain with circuit diagram the working principle of type B chopper.
- c) Explain with circuit diagram the working principle of the circulatory current mode dual converter.
- d) Compare step up and step down chopper on any four points of difference.

#### Q.3) Attempt any Three of the following.

**12 Marks**

- a) Draw circuit diagram of four quadrant chopper and its labeled quadrant diagram.
- b) Describe the operation of McMurray Bedford inverter with circuit diagram.
- c) Draw the circuit diagram of single phase to single phase cyclo converter and sketch the input/output waveforms .

- d) Describe the principle of induction heating with suitable diagram .

**Q.4) Attempt any Three of the following.**

**12 Marks**

- a) Identify a suitable chopper for producing the output in first and fourth quadrant and explain its operation.
- b) Identify the role of the saturable reactor in Morgan chopper. Explain with its circuit diagram.
- c) The applied dc voltage of a type A chopper is 230 V and a load resistance of 10  $\Omega$ . Calculate the average output voltage if duty cycle is 0.4.
- d) Draw input and output waveforms of cycloconverter to produce  $1/4^{\text{th}}$  of input frequency. Show the firing sequence of thyristors in the relevant waveform.
- e) Describe the operation of dual converter with labelled quadrant diagram..

**Q.5) Attempt any Two of the following.**

**12 Marks**

- a) Explain with neat labeled sketch the speed control of DC servo motor.
- b) Identify a suitable Ac voltage stabilizer that uses relays. Describe its operation with diagram.
- c) Identify a suitable type of heating method to heat nonconducting material. Explain its operation with diagram.

**Q.6) Attempt any Two of the following.**

**12 Marks**

- a) Justify FCT as a voltage controlled device with characteristics.
  - b) Identify a suitable inverter in which load is connected in series with commutating components. Explain its operation with circuit diagram.
  - c) Explain the operation of McMurray full bridge inverter with circuit diagram.
-

## Scheme - I

### Sample Test Paper - I

**Program Name** : Electrical Engineering Program Group  
**Program Code** : EE/EP/EU  
**Semester** : Fifth  
**Course Title** : Power Electronic Applications (Elective)  
**Max. Marks** : 20

**22527**

**Time: 1 Hour**

---

**Instructions:**

- (1) All questions are compulsory.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Sub-questions in a main question carry equal marks.
- (5) Assume suitable data if necessary.
- (6) Preferably, write the answers in sequential order.

**Q.1 Attempt any FOUR.**

**08 Marks**

- a. Define latching current and holding current of SCR.
- b. Draw the symbol of SIT and FCT.
- c. Write the types of chopper.
- d. State the relation between average output voltage and duty cycle of a step up chopper.
- e. Draw a neat circuit diagram of single phase bridge inverter.
- f. List two applications of inverters.

**Q.2 Attempt any THREE.**

**12 Marks**

- a. Explain the operation of IGBT with constructional diagram.
  - b. Describe the working principle of MCT with equivalent circuit.
  - c. Draw a neat circuit diagram of Type C chopper and explain its working.
  - d. Explain the operation of Jones chopper with circuit diagram.
  - e. Describe the operation of three phase bridge inverter with circuit diagram.
-

## Scheme - I

### Sample Test Paper - II

**Program Name** : Electrical Engineering Program Group  
**Program Code** : EE/EP/EU  
**Semester** : Fifth  
**Course Title** : Power Electronic Applications (Elective)  
**Max. Marks** : 20

**22527**

**Time: 1 Hour**

---

**Instructions:**

- (1) All questions are compulsory.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Sub-questions in a main question carry equal marks.
- (5) Assume suitable data if necessary.
- (6) Preferably, write the answers in sequential order.

**Q.1 Attempt any FOUR.**

**08 Marks**

- a. State the effect of reactor in circulating current mode dual converter.
- b. State the effect of firing angle in dual converter.
- c. Write any two applications of cycloconverter.
- d. State the need of AC voltage stabilizer.
- e. Write any two advantages of each of the following: i) induction heating and ii) dielectric heating.
- f. Draw a neat circuit diagram of AC circuit breaker.

**Q.2 Attempt any THREE.**

**12 Marks**

- a. Describe the operation of three phase to single phase cycle converter with neat circuit diagram.
  - b. Explain the operation of McMurray half bridge inverter with circuit diagram .
  - c. Explain the operation of closed loop control method for AC servo motor with neat circuit diagram.
  - d. Explain with neat sketches the operation of electric welding control.
  - e. Compare induction heating and dielectric heating on any four points.
-