

22529

**11920**

**3 Hours / 70 Marks**

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.

**Marks**

**1. Attempt any FIVE of the following :**

**10**

- (a) Draw equivalent circuit of alternator.
- (b) Define impedance diagram and reactance diagram.
- (c) List out factors affecting proximity effect.
- (d) State the impact of inductance and resistance on transmission line performance.
- (e) Give the expression for ABCD constant of T model.
- (f) Determine ABCD constant of short transmission line having impedance  $(20 + j50)\Omega$ .
- (g) Recall X & Y coordinates for centre of sending and circle diagram.

2. Attempt any THREE of the following :

12

- (a) Develop a reactance diagram for structure of power system (Refer Fig. 1) considering generator as base.

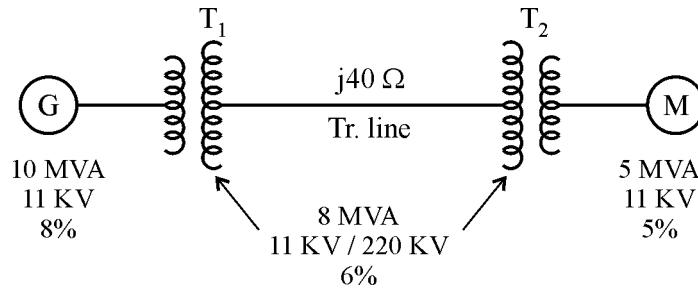


Fig. 2 (a)

- (b) Define self GMD & Mutual GMD with the help of example.
- (c) 3 $\phi$  transmission line with impedance  $32.9 \angle 72.35 \Omega/\text{ph}$  and admittance  $j2.827 \times 10^{-4} \angle 90 \Omega/\text{ph}$  delivers load of 35 MW, 132 KV, 0.8 P.F. lag. Use  $\pi$  method and determine ABCD constants.
- (d) Derive the expression for complex power, active and reactive power at sending end.

3. Attempt any THREE of the following :

12

- (a) Summarise the role of power system engineer.
- (b) Derive the expression for inductance of 3 $\phi$  line with symmetrical arrangement.
- (c) Define Generalised circuit constants.
- (d) A 200 kV line with GCC  $A = 0.86 \angle 7^\circ$ ,  $B = 300 \angle 75^\circ \Omega$ . Determine real power at unity P.F. that can be received if voltage at both end is maintained at 200 kV.

## 4. Attempt any THREE of the following :

12

- (a) Give the stepwise procedure for drawing circle diagram at receiving end.  
 (b) Calculate self GMD for conductors (Refer Fig. 2).

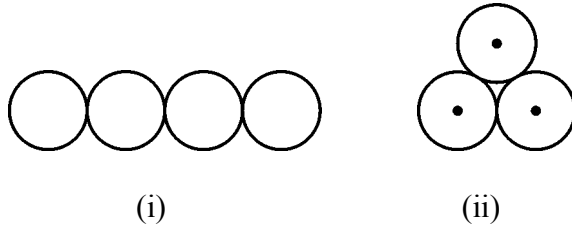


Fig. 4 (b)

- (c) A 3 $\phi$  50 Hz line has resistance of 20  $\Omega$ , inductance 0.2 H and capacitance 1  $\mu$ F. Determine ABCD constants of line considering  $\pi$  model.  
 (d) Derive the condition for maximum power at sending end.  
 (e) 3 $\phi$  line with GCC  $A = 0.99 \angle 0.08^\circ$ ,  $B = 10 + j31.42$ ,  $C = 2.79 \times 10^{-4} \angle 90.04^\circ$  supplies load of 35 MW, 132 kV, 0.8 lag. Determine regulation of line.

## 5. Attempt any TWO of the following :

12

- (a) Determine Inductance & Capacitance of 3 $\phi$  line operating at 50 Hz and conductors are arranged at corners of symmetrical triangle with side 3.4 m & diameter of each conductor is 0.8 cm.  
 (b) A 3 $\phi$  132 kV transmission line delivers 40 MVA at 0.8 pf lag. Draw receiving end circle diagram and determine sending end voltage for  $A = 0.98 \angle 3^\circ$ ,  $B = 140 \angle 78^\circ$ .  
 (c) A 3 $\phi$  line has following parameters  $A = D = 0.9 \angle 0.4^\circ$ ,  $B = 99 \angle 76.86^\circ$  load angle is  $9^\circ$ . If sending end and receiving end voltages are maintained at 220 kV, calculate sending end complex power, active power and reactive power.

**6. Attempt any TWO of the following :****12**

- (a) 3 $\phi$  line has parameter  $A = D = 0.9 \angle 0.4^\circ$ ,  $B = 99 \angle 76.86^\circ$ , sending end & receiving end voltages are maintained at 220 kV. Calculate maximum power supplied at sending end.
- (b) State the necessity of reactive power compensation equipment. List out the devices used for reactive power compensation and give application of each device.
- (c) Prove that  $AD - BC = 1$ .
-