

## Scheme – I

### Sample Question Paper

**Program Name** : Diploma in Digital Electronics  
**Program Code** : DE  
**Semester** : Fifth  
**Course Title** : Digital System Applications  
**Marks** : 70

**22536**

**Time: 3 Hrs.**

---

#### Instructions:

- (1) All questions are compulsory.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data if necessary.
- (5) Preferably, write the answers in sequential order.

#### Q.1 Attempt any FIVE of the following.

**10 Marks**

- a) Draw a 4 bit even parity generator circuit using X-OR gate.
- b) Differentiate between combinational logic circuit and sequential logic circuit.
- c) Draw the state transition diagram for sequence '110' by using Mealy machine.
- d) Define hazards. List its types.
- e) Differentiate between synchronous sequential circuit and asynchronous sequential circuit.
- f) State any two advantages of PLAs.
- g) Draw single decimal digit common anode type display using 7447 decoder and decade counter.

#### Q.2 Attempt any THREE of the following.

**12 Marks**

- a) Use Q-M approach to minimize the function:  
$$F(A, B, C, D, E) = \sum m(0, 1, 2, 7, 9, 11, 12, 23, 27, 28)$$
- b) Design a 16-to-1 multiplexer using two 8-to-1 multiplexers having an active low ENABLE input.
- c) Draw the state transition diagram of two bit up counter.
- d) Draw and describe the block diagram of asynchronous sequential circuit with neat sketch.

**Q.3 Attempt any THREE of the following.****12 Marks**

- a) Design a full subtractor using 3-to-8 decoder and logic gates.
- b) Describe the state reduction method (any one) to design synchronous sequential circuit.
- c) Describe the race condition in asynchronous sequential circuit. Also state method to avoid races.
- d) Draw the internal architecture of PLA device and describe it.

**Q.4 Attempt any THREE of the following.****12 Marks**

- a) Design J K flip flop using T flip flop.
- b) Design S R flip flop using D flip flop.
- c) Design a full adder using PLA.
- d) Describe CPLD with its architecture.
- e) Describe with neat diagram basic instrument to measure time period.

**Q.5 Attempt any two of the following.****12 Marks**

- a) Design a sequence generator for sequence 011 using Moore model and implement using D flip flop.
- b) Design a PLA device to implement a magnitude comparator to produce outputs for  $A_1 A_0$  being equal to, not equal to, less than and greater than  $B_1 B_0$ .
- c) Describe the instrument to measure time with block diagram. Consider unknown input is 200 Hz square wave.

**Q.6 Attempt any two of the following.****12 Marks**

- a) Implement the following Boolean functions with PLA:  
$$F_1(A, B, C) = \sum (0, 1, 2, 4)$$
$$F_2(A, B, C) = \sum (0, 5, 6, 7)$$
- b) Design and draw common anode type single decimal digit display for clock frequency 1 Hz using 7-segment decoder IC 7448 and decade counter.
- c) Design a 4 digit frequency counter using 54/74143 and 54/74160. Use a 1.0 MHz clock and provide 0.1 sec, 1.0 sec and 10 sec gate.

## Scheme – I

### Sample Test Paper - I

**Program Name** : Diploma in Digital Electronics  
**Program Code** : DE  
**Semester** : Fifth  
**Course Title** : Digital System Applications  
**Marks** : 20

**22536**

**Time: 1 Hour.**

#### Instructions:

- (1) All questions are compulsory.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data if necessary.
- (5) Preferably, write the answers in sequential order.

#### Q.1 Attempt any FOUR.

**08 Marks**

- Define decoder. Draw logic diagram for 2-to-4 line decoder.
- Draw a state transition diagram of sequence detector circuit that detects '1101' from input data stream using Mealy model.
- Obtain the state synthesis table for the given (figure 1) state transition diagram of Moore model.

 


Figure 1

- Define static 0 and static 1 hazard.
- Define race condition in digital circuits with suitable example.
- Describe dynamic hazard and its elimination.

**Q.2 Attempt any THREE.**

**12 Marks**

- a) Design a comparator that will compare the two words  $A = (A_1A_0)_2$  and  $B = (B_1B_0)_2$  in binary code.
- b) Reduce the state transition diagram of given figure 2 by Row elimination method or Implication table method.

 


Figure 2

- c) Construct an ASM chart for 2 bit up counter.
- d) State the steps to design asynchronous sequential circuit.
- e) Design SR flip flop using JK flip flop.

## Scheme – I

### Sample Test Paper - II

**Program Name** : Diploma in Digital Electronics  
**Program Code** : DE  
**Semester** : Fifth  
**Course Title** : Digital System Applications  
**Marks** : 20

**22536**

**Time: 1 Hour**

---

#### Instructions:

- (1) All questions are compulsory.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data if necessary.
- (5) Preferably, write the answers in sequential order.

#### Q.1 Attempt any FOUR.

**08 Marks**

- a) State the applications of PLA.
- b) State the difference between PAL and GAL.
- c) Find the value displayed by basic frequency counter if unknown input signal is 7.5 KHz square wave and gate enable time is  $t = 0.1$  sec.
- d) Draw digit control waveform of four digit multiplexed display.
- e) Draw the block diagram of instrument to measure time.
- f) Draw the pin diagram of ADD 3501.

#### Q.2 Attempt any THREE.

**12 Marks**

- a) Compare CPLD and FPGA (any 4 points).
- b) Design the following combinational logic circuit using PLA  
$$Y_1 = \sum m(0, 3, 5, 6, 9, 10, 12, 15)$$
$$Y_2 = \sum m(0, 1, 2, 11, 14, 15)$$
- c) Design and draw common cathode type single decimal digit display for clock frequency 1 Hz using 7-segment decoder IC 7447 and decade counter.
- d) Describe basic frequency counter with neat block diagram.
- e) Describe four decimal digits, period measurement instrument with neat block diagram.