



22629

12223

3 Hours / 70 Marks

Seat No.

| | | | | | | | |
|--|--|--|--|--|--|--|--|
| | | | | | | | |
|--|--|--|--|--|--|--|--|

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks**1. Attempt any FIVE of the following :****10**

- (a) Draw the block diagram of Electric Drive.
- (b) Classify the meters according to duty class.
- (c) Draw the circuit of single phase half-wave SCR converter drive.
- (d) Give the classification of 3 ϕ SCR drives.
- (e) State the need for speed control of AC drives.
- (f) List four specifications of stepper motor.
- (g) List two functions of microprocessor in drives.

2. Attempt any THREE of the following :**12**

- (a) Sketch speed-torque characteristics of three phase induction motor and explain regions of operation.
- (b) Compare 1 ϕ semi-converter drive and 1 ϕ full converter drive on the basis of
 - (i) No. of SCRs
 - (ii) Harmonics
 - (iii) Quadrant operation
 - (iv) Regenerative braking
- (c) Draw and explain the block diagram of class B chopper drive.
- (d) Draw and explain the block diagrams of stator voltage control method using thyristor circuit.



3. **Attempt any THREE of the following :** **12**
- (a) Draw and explain speed torque characteristics of DC shunt and DC series motors.
 - (b) Draw the circuit of 3 ϕ semi-converter drive and state the equation of average armature voltage.
 - (c) Explain the working of class A chopper drive with a neat circuit diagram.
 - (d) List the stages in sugar mills and state the types of motor used at each stage.
4. **Attempt any THREE of the following :** **12**
- (a) Explain the working of Class C chopper drive with a neat circuit diagram.
 - (b) Explain steel rolling mills and the drives used at each stage.
 - (c) Draw the block diagram of V/f control method and explain the working.
 - (d) List four advantages of microprocessor based control for drives.
 - (e) Draw and explain the block diagram of Phase Locked Loop (PLL) control of DC motor.
5. **Attempt any TWO of the following :** **12**
- (a) Explain the working of 1 ϕ dual converter drive with a neat sketch and waveforms.
 - (b) Explain the application of chopper control in solar and battery powered vehicles.
 - (c) Draw the block diagram of microprocessor based control of DC motor and explain it.
6. **Attempt any TWO of the following :** **12**
- (a) A full converter drive operated from single phase 230 V, 50 Hz supply drives a 9 H.P. 200 V, 1500 rpm, separately excited DC motor. The rated armature current is 50 A. Motor parameters $R_a = 0.3 \Omega$, $L_a = 10 \text{ mH}$, $K_a \phi$ constant = 0.2 V/m. Find the (i) average armature voltage (ii) back emf of motor (iii) speed of motor (iv) motor torque of a firing angle of 30° .
 - (b) Explain Class E chopper drive.
 - (c) Explain rotor resistance control using chopper with a neat circuit diagram.

