Seat	
No.	

[5056]-15

## F.E. EXAMINATION, 2016 BASIC ELECTRONICS ENGINEERING (2015 PATTERN)

Time: Two Hours

Maximum Marks: 50

- **N.B.** :— (i) Figures to the right indicate full marks.
  - (ii) Neat diagrams must be drawn wherever necessary.
  - (iii) Use of electronic pocket calculator is allowed.
  - (iv) Assume suitable data, if necessary.
- 1. (a) Draw and explain the V-I characteristics of a Zener diode. What are the two breakdown mechanisms in a Zener diode?
  - (b) What do you understand by a D.C. load line and Q point? Explain their significance. [6]

Or

- 2. (a) For a bridge rectifier, the RMS secondary voltage of transformer is 12.7 V. Assume ideal diodes and  $R_L$  = 1 K $\Omega$ . [6] Find :
  - (i) Peak Current
  - (ii) DC load current
  - (iii) DC load voltage
  - (iv) RMS current
  - (v) Peak Inverse Voltage of diode
  - (vi) RMS Voltage across load.
  - (b) Compare BJT and MOSFET.

[6]

<b>3.</b>	( <i>a</i> )	Define and give typical values of the following op-amp				
		parameters: [6]				
		(i) Voltage Gain				
		(ii) CMRR				
		(iii) Slew Rate.				
( <i>b</i> )		What is meant by Universal Gate ? By using any universal				
		gate draw AND, OR, NOT basic gates. [5]				
	(c)	What do you mean by counter ? State different types of				
		counters. [2]				
	Or					
4.	(a)	Draw a circuit diagram of an Op-Amp as an integrator and				
		derive the expression for its output voltage. [6]				
	( <i>b</i> )	What is multiplexer ? Explain one with example. Write its				
		relation between select lines and input lines. [7]				
<b>5.</b>	(a) Draw block diagram of Electronic Weighing Machine and e					
		its operation. [6]				
	( <i>b</i> )	Explain the construction and characteristics of SCR. [6]				
Or						
6.	(a)	Explain the construction and working of LVDT with neat				
		diagram. [6]				
	( <i>b</i> )	Compare the three types of Temperature Transducers. [6]				
[5056	3]-15	2				

<b>7</b> .	(a)	What is need of modulation? Explain Amplitude Modul	ation
		in detail.	[7]
	( <i>b</i> )	Draw and explain block diagram of GSM system.	[6]
		Or	
8.	(a)	Draw and explain electromagnetic spectrum.	[5]
	( <i>b</i> )	Explain the following things about FM:	[8]
		(i) Deviation ratio	
		(ii) Mathematical representation of FM	
		(iii) Advantages and Disadvantages	
		(iv) Modulation index.	